

Microwave Engineering


EC 401

DoECE

Sardar Vallabhbhai National Institute Of
Technplogy



Module 4

Power Dividers and Circulators

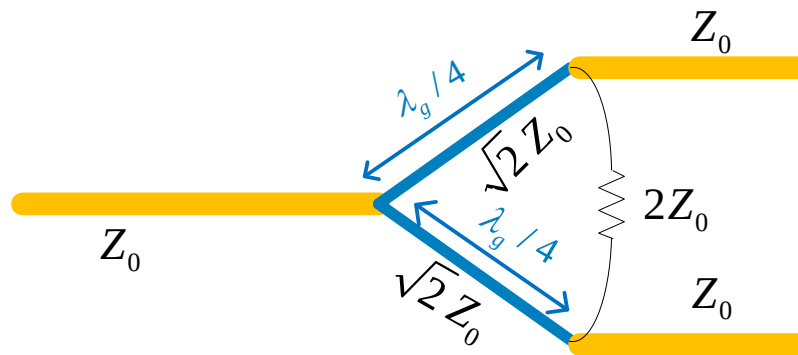


Power Dividers

Power Divider and Combiner/Coupler

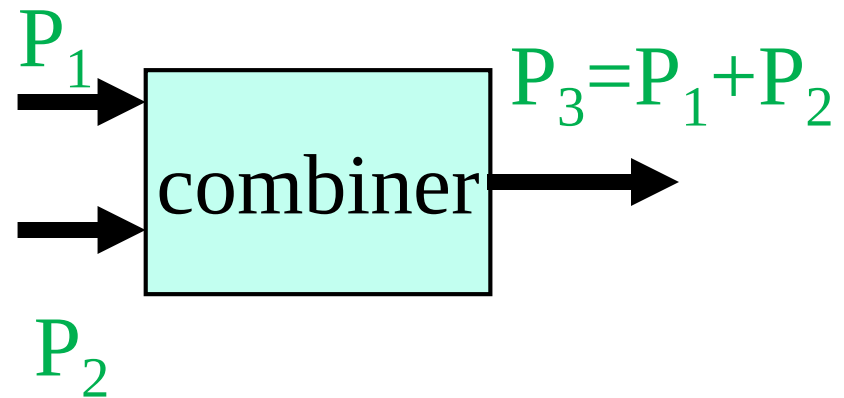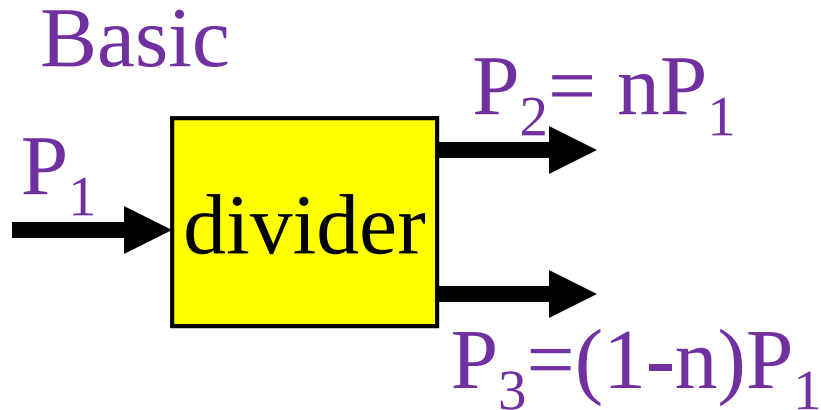

Divide into 4 output

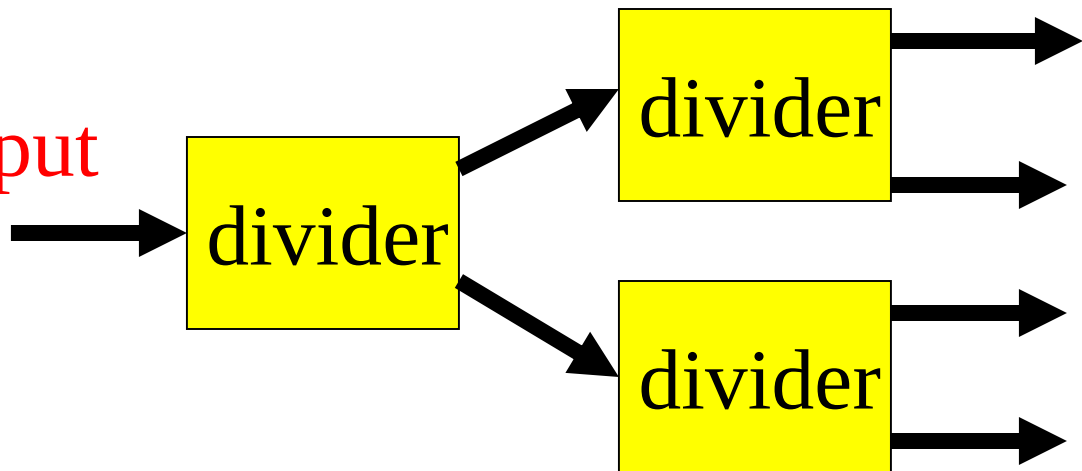

- ❖ A power divider is used to split a signal.
- ❖ A coupler is used to combine a signal.

LOSSLESS NETWORK

For lossless n-network,
total input power = total output power.


Thus $\underbrace{\sum_{i=1}^n a_i a_i^*}_{a^t a^*} = \underbrace{\sum_{i=1}^n b_i b_i^*}_{b^t b^*}$

Where a and b are the
amplitude of the signal

Putting in matrix form $a^t a^* = b^t b^* = a^t S^t S^* a^*$

Note that $b^t = a^t S^t$ and $b^* = S^* a^*$

Thus $a^t (U - S^t S^*) a^* = 0$

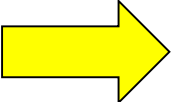 This implies that $S^t S^* = U$

RECIPROCAL AND SYMMETRICAL NETWORK

U is called unitary matrix $[U] = [U]^t$

In summation form $\sum_{k=1}^n S_{ki} S_{kj}^* = \begin{cases} 1 & \text{for } i = j \\ 0 & \text{for } i \neq j \end{cases}$

For reciprocal network

$[Z] = [Z]^t \rightarrow$ Since $[Z]$ is symmetry

Thus it can be shown that $[S] = [S]^t$

Properties of the S Matrix

For reciprocal networks (networks containing only reciprocal materials), the S -matrix is symmetric:

$$S_{ij} = S_{ji} \quad i \neq j$$

$$\Rightarrow [S] = [S]^T$$

Example of a nonreciprocal material: a biased ferrite

EXAMPLE

A certain two-port network is measured and the following scattering matrix is obtained:

$$[S] = \begin{bmatrix} 0.1 \angle 0^\circ & 0.8 \angle 90^\circ \\ 0.8 \angle 90^\circ & 0.2 \angle 0^\circ \end{bmatrix}$$

- ❖ From the data , determine whether the network is reciprocal or lossless.
- ❖ If a short circuit is placed on port 2, what will be the resulting return loss at port 1?

EXAMPLE

Solution: $[S] = \begin{bmatrix} 0.1 \angle 0^\circ & 0.8 \angle 90^\circ \\ 0.8 \angle 90^\circ & 0.2 \angle 0^\circ \end{bmatrix}$

Since $[S]$ is symmetry, the network is reciprocal.

To be lossless, the S parameters must satisfy

$$\left. \sum_{k=1}^n S_{ki} S_{kj}^* = \begin{cases} 1 & \text{for } i = j \\ 0 & \text{for } i \neq j \end{cases} \right\} \quad \text{For } i=j$$

$$|S_{11}|^2 + |S_{12}|^2 = (0.1)^2 + (0.8)^2 = 0.65 \neq 1$$

Thus, it is not a lossless network.

EXAMPLE (CONTD.)

Reflected power at port 1 and port 2:

$a_2 = -b_2$ for port 2 being short circuited


$$b_1 = S_{11}a_1 + S_{12}a_2 = S_{11}a_1 - S_{12}b_2 \quad (1)$$

$$b_2 = S_{21}a_1 + S_{22}a_2 = S_{21}a_1 - S_{22}b_2 \quad (2)$$

From (2) we have

$$b_2 = \frac{S_{21}}{1 + S_{22}} a_1 \quad (3)$$

Short at port 2

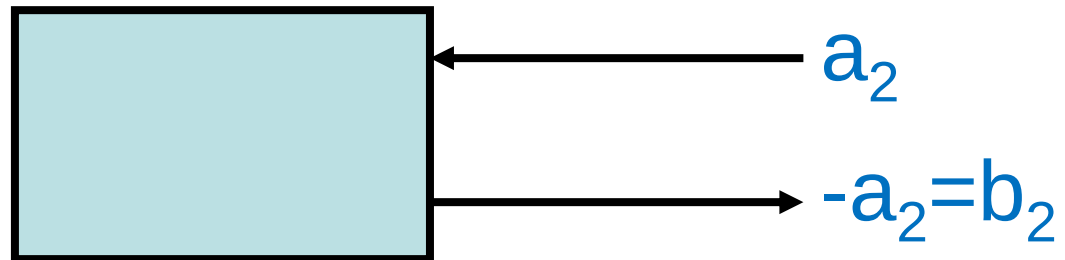

EXAMPLE (CONTD.)

Dividing (1) by a_1 and substitute the result in (3) ,we have

$$\begin{aligned}\rho &= \frac{b_1}{a_1} = S_{11} - S_{12} \frac{b_2}{a_1} = S_{11} - \frac{S_{12} S_{21}}{1 + S_{22}} \\ &= 0.1 - \frac{(j0.8)(j0.8)}{1 + 0.2} = 0.633\end{aligned}$$

Return loss

$$-20\log \rho = -20\log(0.633) = 3.97 \text{ dB}$$

S-parameter For Power Divider/Coupler

Generally $[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{32} & S_{33} \end{bmatrix}$

For reciprocal and lossless network

$$\sum_{k=1}^N S_{ki} S_{ki}^* = 1$$

$$\sum_{k=1}^N S_{ki} S_{kj}^* = 0 \quad \text{for } i \neq j$$

$$|S_{11}|^2 + |S_{12}|^2 + |S_{13}|^2 = 1$$

$$\text{Row 1x row 2} \rightarrow S_{11}S_{21}^* + S_{12}S_{22}^* + S_{13}S_{23}^* = 0$$

$$|S_{21}|^2 + |S_{22}|^2 + |S_{23}|^2 = 1$$

$$\text{Row 2x row 3} \rightarrow S_{21}S_{31}^* + S_{22}S_{32}^* + S_{23}S_{33}^* = 0$$

$$|S_{31}|^2 + |S_{32}|^2 + |S_{33}|^2 = 1$$

$$\text{Row 1x row 3} \rightarrow S_{11}S_{31}^* + S_{12}S_{32}^* + S_{13}S_{33}^* = 0$$

Three Port Networks (cont.)

If all ports are matched properly , then $S_{ii} = 0$

For Reciprocal network

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & 0 \end{bmatrix}$$

For lossless network, must satisfy unitary condition

$$\begin{aligned} |S_{12}|^2 + |S_{13}|^2 &= 1 & S_{13}^* S_{23} &= 0 \\ |S_{12}|^2 + |S_{23}|^2 &= 1 & S_{23}^* S_{12} &= 0 \\ |S_{13}|^2 + |S_{23}|^2 &= 1 & S_{12}^* S_{13} &= 0 \end{aligned}$$

- ❖ Two of (S_{12}, S_{13}, S_{23}) must be zero but it is not consistent.
- ❖ If $S_{12} = S_{13} = 0$, then S_{23} should equal to 1 and the first equation will not equal to 1.
- ❖ This is invalid.

Implying that a three-port network cannot be simultaneously lossless, reciprocal, and matched at all ports.

Nonreciprocal Network (Apply For Circulator)

For Nonreciprocal and matched at all ports

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{21} & 0 & S_{23} \\ S_{31} & S_{32} & 0 \end{bmatrix} \quad \Rightarrow$$

For lossless network, must satisfy unitary condition

$$|S_{12}|^2 + |S_{13}|^2 = 1 \quad S_{31}^* S_{32} = 0$$

$$|S_{21}|^2 + |S_{23}|^2 = 1 \quad S_{21}^* S_{23} = 0$$

$$|S_{31}|^2 + |S_{32}|^2 = 1 \quad S_{12}^* S_{13} = 0$$

The above equations must satisfy the following either


$$S_{12} = S_{23} = S_{31} = 0 \quad |S_{21}| = |S_{32}| = |S_{13}| = 1$$

or


$$S_{21} = S_{32} = S_{13} = 0 \quad |S_{12}| = |S_{23}| = |S_{31}| = 1$$

Circulator (Nonreciprocal Network)
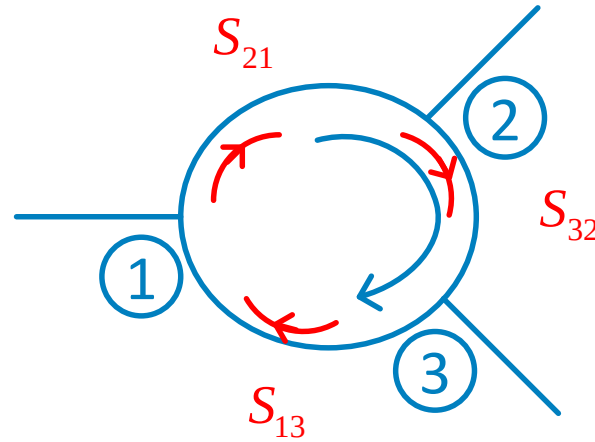
$$[S] = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix}$$


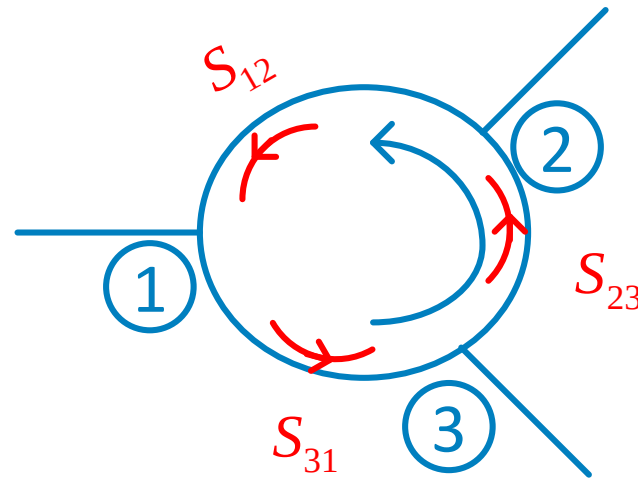
$$[S] = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \end{bmatrix}$$



We can demonstrate here that any matched lossless three-port network must be nonreciprocal and, thus, a circulator.

Another Alternative For Reciprocal Network

Only two ports are matched , then for lossless and reciprocal network

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & S_{33} \end{bmatrix}$$

For lossless network, must satisfy unitary condition

$$|S_{12}|^2 + |S_{13}|^2 = 1$$

$$S_{13}^* S_{23} = 0$$

$$|S_{12}|^2 + |S_{23}|^2 = 1$$

$$S_{12}^* S_{13} + S_{23}^* S_{33} = 0$$


$$|S_{13}|^2 + |S_{23}|^2 + |S_{33}|^2 = 1$$

$$S_{23}^* S_{12} + S_{33}^* S_{13} = 0$$

The two equations show
that $|S_{13}| = |S_{23}|$
thus $S_{13} = S_{23} = 0$
and $|S_{12}| = |S_{33}| = 1$
These have satisfied all

RECIPROCAL LOSSLESS NETWORK OF TWO MATCHED
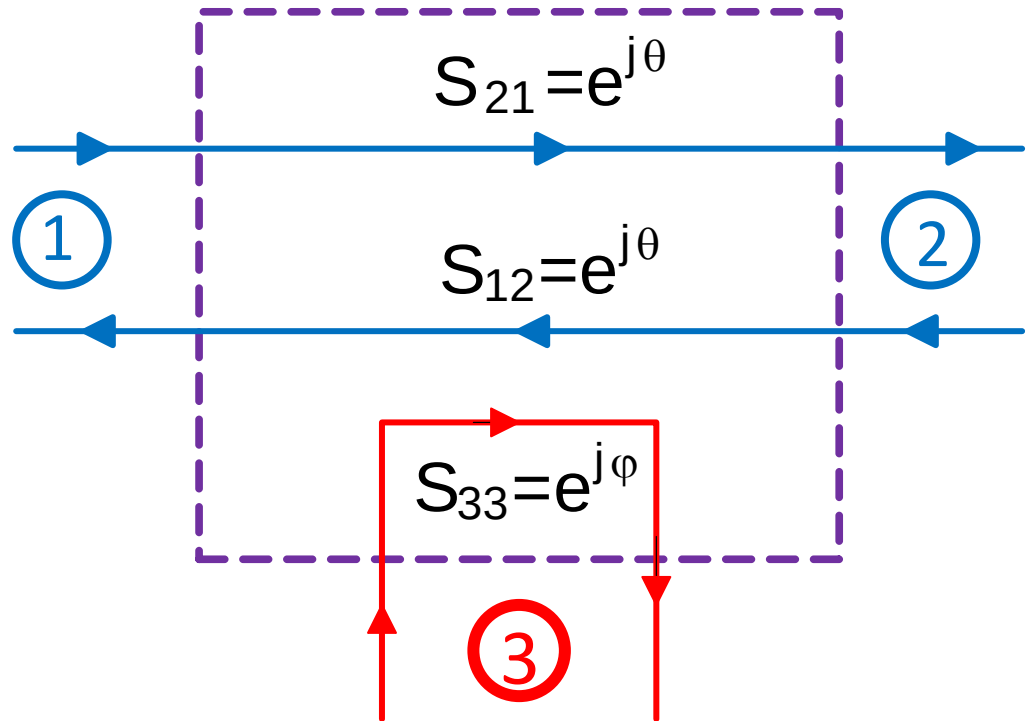
$$[S] = \begin{bmatrix} 0 & e^{j\theta} & 0 \\ e^{j\theta} & 0 & 0 \\ 0 & 0 & e^{j\phi} \end{bmatrix}$$



Two port network with third port are isolated

RECIPROCAL LOSSY NETWORK OF ALL PORTS MATCHED

- ❖ Finally, if the three-port network is allowed to be lossy, it can be reciprocal and matched at all ports;
- ❖ This is the case of the *resistive divider*
- ❖ In addition, a lossy three-port network can be made to have isolation between its output ports (e.g., $S_{23} = S_{32} = 0$).

Three Port Networks (cont.)


1) Not possible → **Lossless** **Reciprocal**
All ports matched

2) Circulator → **Lossless** **Non Reciprocal**
All ports matched

3) Lossless power divider → **Lossless** **Reciprocal**
One port matched

Three Port Networks (cont.)

4) Lossy power divider

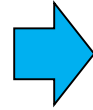


Lossy

Reciprocal

All ports matched

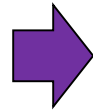5) Two port network with third port are isolated



Lossless

Reciprocal

Two ports matched

FOUR PORT NETWORK

Generally

$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} & S_{14} \\ S_{21} & S_{22} & S_{23} & S_{24} \\ S_{31} & S_{32} & S_{33} & S_{34} \\ S_{41} & S_{42} & S_{43} & S_{44} \end{bmatrix}$$

For reciprocal and lossless network

$$\sum_{k=1}^N S_{ki} S_{ki}^* = 1$$

$$\sum_{k=1}^N S_{ki} S_{kj}^* = 0 \quad \text{for } i \neq j$$

$ S_{11} ^2 + S_{12} ^2 + S_{13} ^2 + S_{14} ^2 = 1$	R 1x R 2	$S_{11}S_{21}^* + S_{12}S_{22}^* + S_{13}S_{23}^* + S_{14}S_{24}^* = 0$
$ S_{21} ^2 + S_{22} ^2 + S_{23} ^2 + S_{24} ^2 = 1$	R1x R3	$S_{11}S_{31}^* + S_{12}S_{32}^* + S_{13}S_{33}^* + S_{14}S_{34}^* = 0$
$ S_{31} ^2 + S_{32} ^2 + S_{33} ^2 + S_{34} ^2 = 1$	R1x R4	$S_{11}S_{41}^* + S_{12}S_{42}^* + S_{13}S_{43}^* + S_{14}S_{44}^* = 0$
$ S_{41} ^2 + S_{42} ^2 + S_{43} ^2 + S_{44} ^2 = 1$	R 2x R3	$S_{21}S_{31}^* + S_{22}S_{32}^* + S_{23}S_{33}^* + S_{24}S_{34}^* = 0$
	R2x R4	$S_{21}S_{41}^* + S_{22}S_{42}^* + S_{23}S_{43}^* + S_{24}S_{44}^* = 0$
	R3x R4	$S_{31}S_{41}^* + S_{32}S_{42}^* + S_{33}S_{43}^* + S_{34}S_{44}^* = 0$

MATCHED FOUR PORT NETWORK

Say all ports are matched and symmetrical network, then

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} & S_{14} \\ S_{12} & 0 & S_{23} & S_{24} \\ S_{13} & S_{23} & 0 & S_{34} \\ S_{14} & S_{24} & S_{34} & 0 \end{bmatrix}$$

The unitarity condition become

$$|S_{12}|^2 + |S_{13}|^2 + |S_{14}|^2 = 1$$

$$|S_{12}|^2 + |S_{23}|^2 + |S_{24}|^2 = 1$$

$$|S_{13}|^2 + |S_{23}|^2 + |S_{34}|^2 = 1$$

$$|S_{14}|^2 + |S_{24}|^2 + |S_{34}|^2 = 1$$

$$\text{R 1x R 2} \quad S_{13}S_{23}^* + S_{14}S_{24}^* = 0 \quad 1$$

$$\text{R1x R3} \quad S_{12}S_{23}^* + S_{14}S_{34}^* = 0 \quad 2$$

$$\text{R1x R4} \quad S_{12}S_{24}^* + S_{13}S_{34}^* = 0 \quad 3$$

$$\text{R 2x R3} \quad S_{12}S_{13}^* + S_{24}S_{34}^* = 0 \quad 4$$

$$\text{R2x R4} \quad S_{12}S_{14}^* + S_{23}S_{34}^* = 0 \quad 5$$

$$\text{R3x R4} \quad S_{13}S_{14}^* + S_{23}S_{24}^* = 0 \quad 6$$

TO CHECK VALIDITY

Multiply eq. 1 by S_{24}^* and eq. 6 by S_{13}^* , and subtract to obtain

$$S_{14}^* \left(|S_{13}|^2 - |S_{14}|^2 \right) = 0 \quad 7$$

Multiply eq. 5 by S_{34} and eq. 4 by S_{13} , and subtract to obtain

$$S_{23} \left(|S_{12}|^2 - |S_{34}|^2 \right) = 0 \quad 8$$

- ❖ Both equations 7 and 8 will be satisfy if $S_{14} = S_{23} = 0$.
- ❖ This means that no coupling between port 1 and 4, and between port 2 and 3 as happening in most directional couplers.

ABCD TO S-PARAMETERS

$$S_{11} = \frac{A + \frac{B}{Z_o} - Z_o C - D}{A + \frac{B}{Z_o} + Z_o C + D}$$

For Symmetrical Network

$$S_{11} = S_{22} \quad (A = D)$$

$$S_{12} = \frac{2(AD - BC)}{A + \frac{B}{Z_o} + Z_o C + D}$$

For Reciprocal Network

$$S_{12} = S_{21}$$

$$S_{21} = \frac{2}{A + \frac{B}{Z_o} + Z_o C + D}$$

$$AD - BC = 1$$

$$S_{22} = \frac{-A + \frac{B}{Z_o} - Z_o C + D}{A + \frac{B}{Z_o} + Z_o C + D}$$

Directional Coupler

If all ports matched , symmetry and $S_{14}=S_{23}=0$ to be satisfied

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} & 0 \\ S_{12} & 0 & 0 & S_{24} \\ S_{13} & 0 & 0 & S_{34} \\ 0 & S_{24} & S_{34} & 0 \end{bmatrix}$$

The equations reduce to 6 equations

$$S_{12}S_{24}^* + S_{13}S_{34}^* = 0$$

$$S_{12}S_{13}^* + S_{24}S_{34}^* = 0$$

i $|S_{12}|^2 + |S_{13}|^2 = 1$

ii $|S_{12}|^2 + |S_{24}|^2 = 1$

iii $|S_{13}|^2 + |S_{34}|^2 = 1$

iv $|S_{24}|^2 + |S_{34}|^2 = 1$

By comparing equations i and ii yield $|S_{13}| = |S_{24}|$

By comparing equations ii and iii yield $|S_{12}| = |S_{34}|$

Directional Coupler (Contd.)

Simplified by choosing $S_{12} = S_{34} = \alpha$; $S_{13} = \beta e^{j\theta}$ and $S_{24} = \beta e^{j\varphi}$

R 2x R3 $S_{12}S_{13}^* + S_{24}S_{34}^* = 0$

➡ Where $\theta + \varphi = \pi \pm 2n\pi$

2 cases

1. Symmetry Coupler $\theta = \varphi = \pi/2$

2. Antisymmetry Coupler

$$\theta = 0, \varphi = \pi$$

Both satisfy


$$\alpha^2 + \beta^2 = 1$$

$$[S] = \begin{bmatrix} 0 & \alpha & j\beta & 0 \\ \alpha & 0 & 0 & j\beta \\ j\beta & 0 & 0 & \alpha \\ 0 & j\beta & \alpha & 0 \end{bmatrix}$$

$$[S] = \begin{bmatrix} 0 & \alpha & \beta & 0 \\ \alpha & 0 & 0 & -\beta \\ \beta & 0 & 0 & \alpha \\ 0 & -\beta & \alpha & 0 \end{bmatrix}$$

PHYSICAL INTERPRETATION

$$|S_{12}|^2 = \text{power deliver to port 2} = \alpha^2 = 1 - \beta^2$$

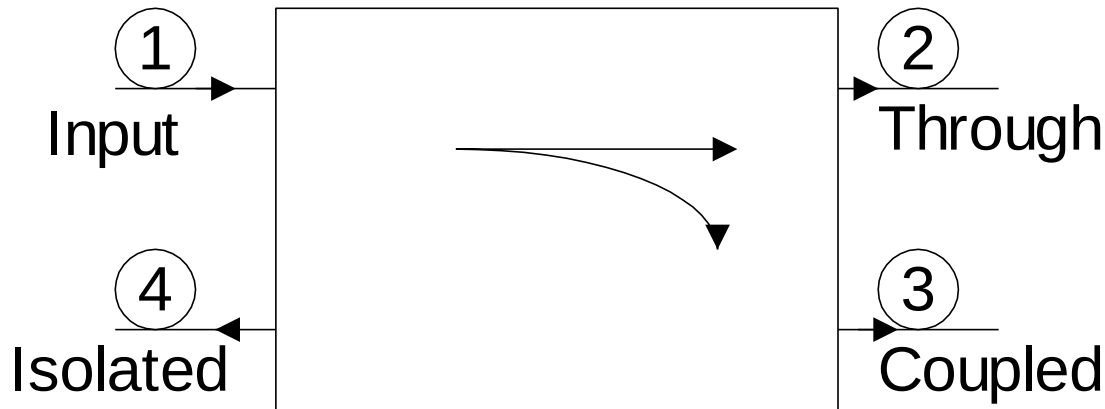

$$|S_{13}|^2 = \text{coupling factor} = \beta^2$$

Characterization of coupler

Coupling = $C = 10 \log \frac{P_1}{P_3} = -20 \log \beta \quad \text{dB}$

Directivity = $D = 10 \log \frac{P_3}{P_4} = -20 \log \frac{\beta}{|S_{14}|} \quad \text{dB}$

Isolation = $I = 10 \log \frac{P_1}{P_4} = -20 \log |S_{14}| \quad \text{dB}$

$$I = D + C \quad \text{dB}$$

For ideal case
 $|S_{14}| = 0$

PRACTICAL COUPLER

Hybrid 3 dB couplers

$$\theta = \varphi = \pi/2$$

$$\alpha = \beta = 1/\sqrt{2}$$

$$[S] = \frac{1}{\sqrt{2}} \begin{bmatrix} 0 & 1 & j & 0 \\ 1 & 0 & 0 & j \\ j & 0 & 0 & 1 \\ 0 & j & 1 & 0 \end{bmatrix}$$

Magic -T and Rat-race couplers

$$\theta = 0, \varphi = \pi$$


$$\alpha = \beta = 1/\sqrt{2}$$

$$[S] = \frac{1}{\sqrt{2}} \begin{bmatrix} 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & -1 \\ 1 & 0 & 0 & 1 \\ 0 & -1 & 1 & 0 \end{bmatrix}$$


T-JUNCTION POWER DIVIDER

- ❖ The T-junction power divider is a simple three-port network that can be used for power division or power combining.
- ❖ It can be implemented in virtually any type of transmission line medium.


T-JUNCTION POWER DIVIDER

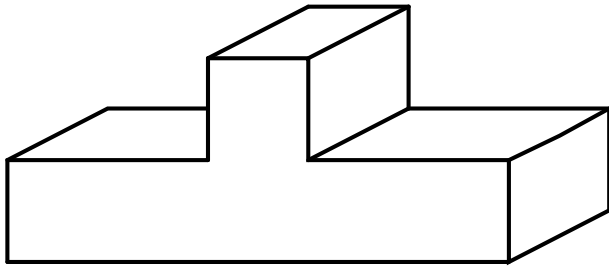

E-plane T

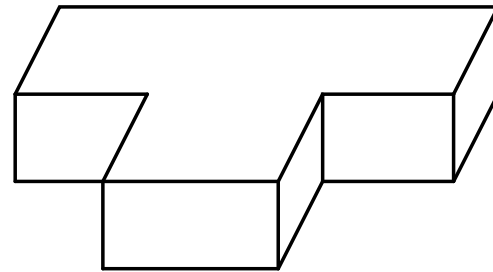


H-plane T

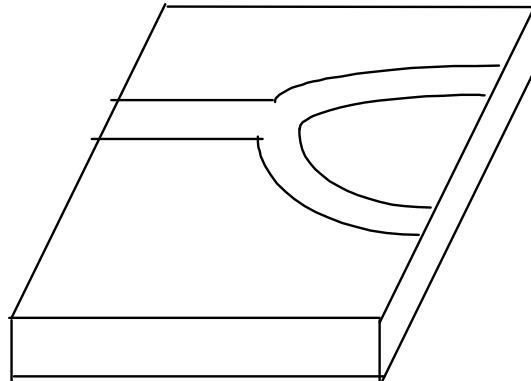

Microstrip T

LOSSLESS DIVIDER

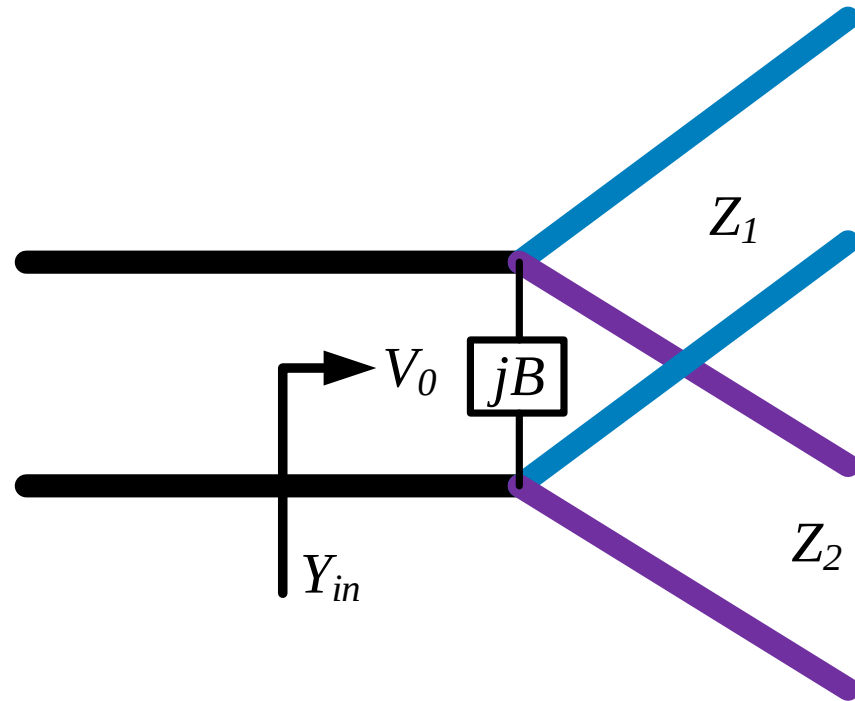

The lossless T-junctions of Figure can all be modeled as a junction of three transmission lines, as shown in Figure.

T-MODEL

- The fringing fields and higher order modes associated with the discontinuity at such a junction, leading to stored energy that can be accounted for by a lumped susceptance, B .
- In order for the divider to be matched to the input line of characteristic impedance Z_0 , we must have

$$\text{Lossy line } Y_{in} = jB + \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{Z_0} \qquad \text{Lossless line } Y_{in} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

- In practice, if B is not negligible, some type of reactive tuning element can usually be added to the divider to cancel this susceptance, at least over a narrow frequency range.


If $Z_o = 50$, then for equally divided power, $Z_1 = Z_2 = 100$

Power Dividers

T-Junction: A lossless divider

$$Y_{in_1} = \frac{1}{Z_{02}} + \frac{1}{Z_{03}}$$

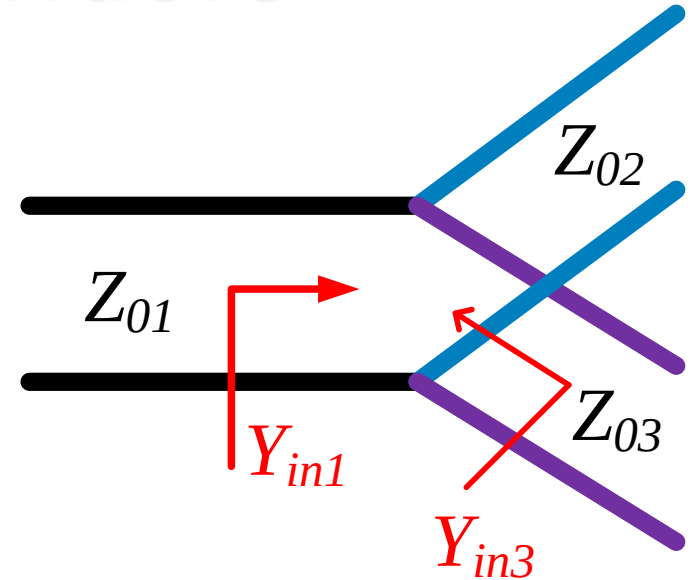To match: $Z_{01} = Z_{in_1} = \frac{1}{Y_{in_1}} = Z_{02} \parallel Z_{03} = \frac{Z_{02}Z_{03}}{Z_{02} + Z_{03}}$



We then have: $Y_{in_3} = \frac{1}{Z_{01}} + \frac{1}{Z_{02}} = \frac{Z_{02} + Z_{03}}{Z_{02}Z_{03}} + \frac{1}{Z_{02}} = \frac{Z_{02} + 2Z_{03}}{Z_{02}Z_{03}} = \frac{1}{Z_{03}} \left(\frac{Z_{02} + 2Z_{03}}{Z_{02}} \right)$

Thus, $Y_{in_3} \neq \frac{1}{Z_{03}}$

Similarly, $Y_{in_2} \neq \frac{1}{Z_{02}}$

If we match at port 1, we cannot match at the other ports!

Note: Matching at ports 2 and 3 would be helpful when output lines 2 and 3 are not matched to their loads.

Power Dividers (cont.)


Assuming port 1 matched:

$$Z_{01} = \frac{Z_{02} Z_{03}}{Z_{02} + Z_{03}}$$

$$P_{in_1} = \frac{1}{2} \frac{|V_1|^2}{Z_{01}}$$

$$P_{out_2} = \frac{1}{2} \frac{|V_1|^2}{Z_{02}} = \frac{Z_{01}}{Z_{02}} P_{in_1}$$

$$P_{out_3} = \frac{1}{2} \frac{|V_1|^2}{Z_{03}} = \frac{Z_{01}}{Z_{03}} P_{in_1}$$

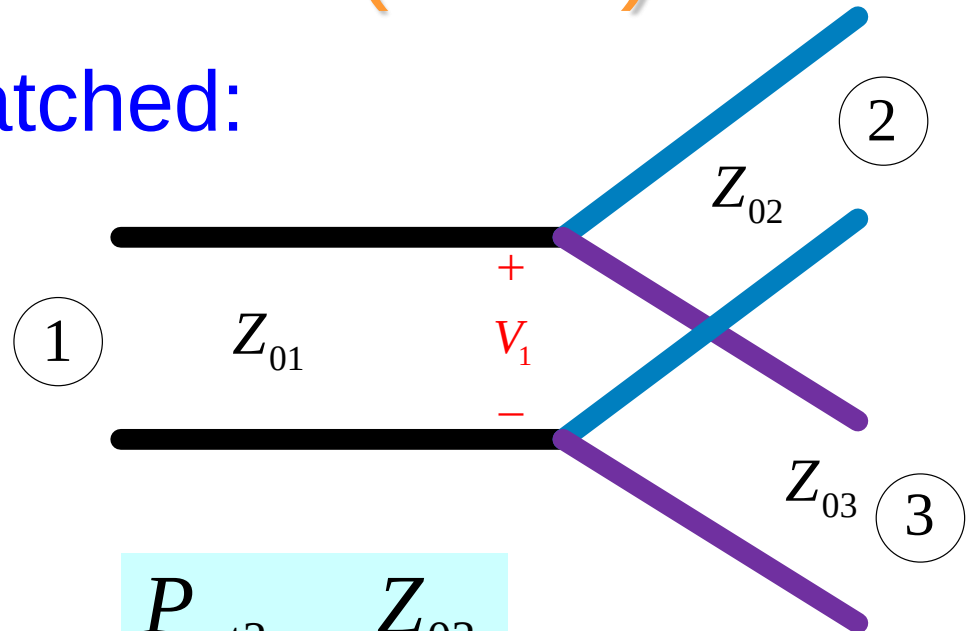

$$\frac{P_{out2}}{P_{out3}} = \frac{Z_{03}}{Z_{02}}$$

We can design the splitter to control the powers going into the two output lines.

For Equal power divider, $Z_{02}=Z_{03}=2Z_{01}$


Power Dividers (cont.)

Examine the reflection at each port (S_{ii}):

$$S_{11} = \left. \frac{V_1^- / \sqrt{Z_{01}}}{V_1^+ / \sqrt{Z_{01}}} \right|_{a_2=a_3=0} = \left. \frac{V_1^-}{V_1^+} \right|_{a_2=a_3=0}$$

$$= \frac{Z_{in1} - Z_{01}}{Z_{in1} + Z_{01}} = \frac{Z_{02} \parallel Z_{03} - Z_{01}}{Z_{02} \parallel Z_{03} + Z_{01}}$$
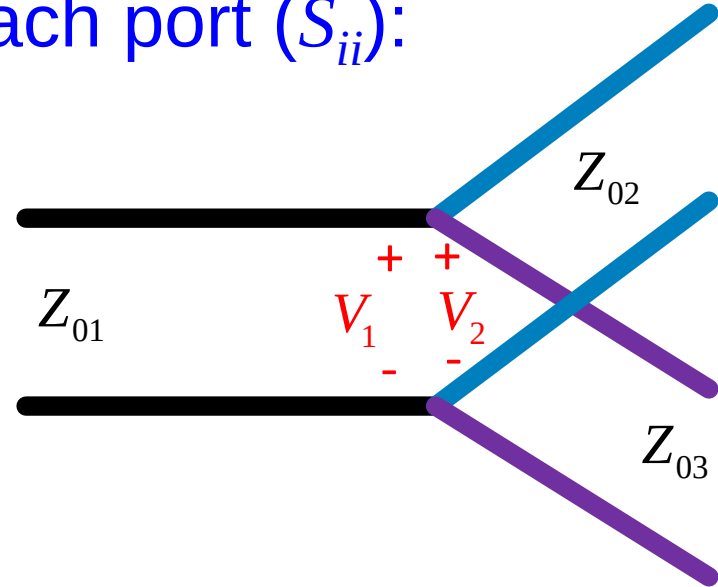
$$= 0 \quad (\text{zero if port 1 is matched})$$



Note: A match on port 1 requires:

$$Z_{01} < Z_{02}, \quad Z_{01} < Z_{03}$$

(The two output lines combine in parallel.)

$$S_{22} = \left. \frac{V_2^-}{V_2^+} \right|_{a_1=a_3=0}$$

$$= \frac{Z_{01} \parallel Z_{03} - Z_{02}}{Z_{01} \parallel Z_{03} + Z_{02}}$$

$$S_{33} = \left. \frac{V_3^-}{V_3^+} \right|_{a_1=a_2=0}$$

$$= \frac{Z_{01} \parallel Z_{02} - Z_{03}}{Z_{01} \parallel Z_{02} + Z_{03}}$$

The first term in the numerators must be less than the second term. $\Rightarrow S_{22} \neq 0, \quad S_{33} \neq 0$

Power Dividers (cont.)

Also, we have:

$$S_{21} = \left. \frac{\frac{V_2^-}{\sqrt{Z_{02}}}}{\frac{V_1^+}{\sqrt{Z_{01}}}} \right|_{a_2=a_3=0} = \frac{V_2^-}{V_1^+} \sqrt{\frac{Z_{01}}{Z_{02}}}$$


$$V_2^- / V_1^+ = V_2 / V_1^+ = V_1 / V_1^+$$

Also

$$V_1 = V_1^+ (1 + S_{11}) \Rightarrow V_1 / V_1^+ = (1 + S_{11})$$

Hence
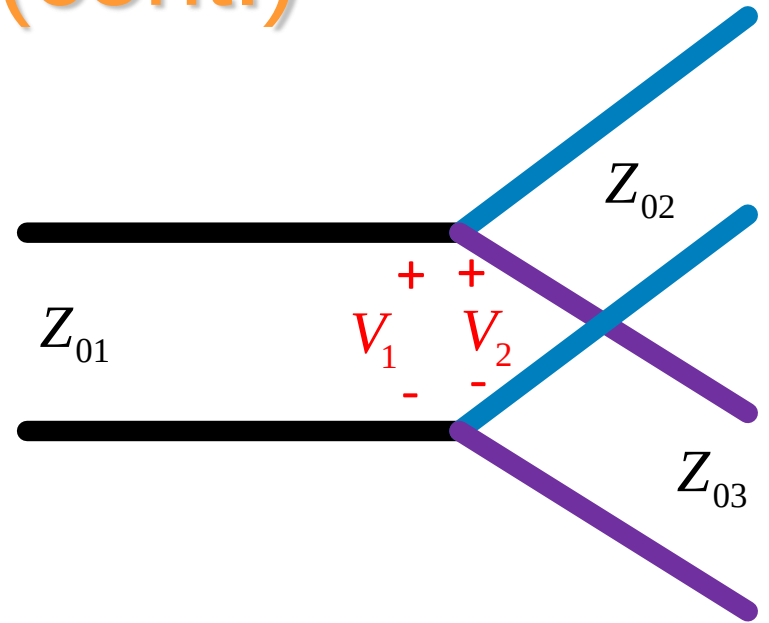
$$S_{21} = (1 + S_{11}) \sqrt{\frac{Z_{01}}{Z_{02}}} = S_{12}$$



Similarly:

$$S_{31} = (1 + S_{11}) \sqrt{\frac{Z_{01}}{Z_{03}}} = S_{13}$$

$$S_{32} = S_{23} = (1 + S_{22}) \sqrt{\frac{Z_{02}}{Z_{03}}}$$

Power Dividers (cont.)

If port 1 is matched: $Z_{01} = \frac{Z_{02}Z_{03}}{Z_{02} + Z_{03}}$

$$\Rightarrow S_{11} = 0 ; \quad S_{22} = \frac{Z_{01} \parallel Z_{03} - Z_{02}}{Z_{01} \parallel Z_{03} + Z_{02}} ; \quad S_{33} = \frac{Z_{01} \parallel Z_{02} - Z_{03}}{Z_{01} \parallel Z_{02} + Z_{03}}$$

The output ports 2 and 3 are not Matched.

$$S_{21} = S_{12} = (1 + S_{11}) \sqrt{\frac{Z_{01}}{Z_{02}}} = \sqrt{\frac{Z_{01}}{Z_{02}}} = \sqrt{\frac{Z_{03}}{Z_{02} + Z_{03}}}$$

$$S_{31} = S_{13} = (1 + S_{11}) \sqrt{\frac{Z_{01}}{Z_{03}}} = \sqrt{\frac{Z_{01}}{Z_{03}}} = \sqrt{\frac{Z_{02}}{Z_{02} + Z_{03}}}$$

$$[S] = \begin{pmatrix} 0 & S_{12} & S_{13} \\ S_{12} & S_{22} & S_{23} \\ S_{13} & S_{23} & S_{33} \end{pmatrix}$$

From last slide: $S_{32} = S_{23} = (1 + S_{22}) \sqrt{\frac{Z_{02}}{Z_{03}}}$

Only $S_{11} = 0$

The output ports 2 and 3 are not isolated.

Power Dividers (cont.)

Summary


$$Z_{01} = \frac{Z_{02} Z_{03}}{Z_{02} + Z_{03}}$$

$$S_{11} = 0 ; \quad S_{22} = \frac{Z_{01} \parallel Z_{03} - Z_{02}}{Z_{01} \parallel Z_{03} + Z_{02}} ; \quad S_{33} = \frac{Z_{01} \parallel Z_{02} - Z_{03}}{Z_{01} \parallel Z_{02} + Z_{03}}$$

$$S_{21} = S_{12} = \sqrt{\frac{Z_{03}}{Z_{02} + Z_{03}}}$$

$$S_{31} = S_{13} = \sqrt{\frac{Z_{02}}{Z_{02} + Z_{03}}}$$
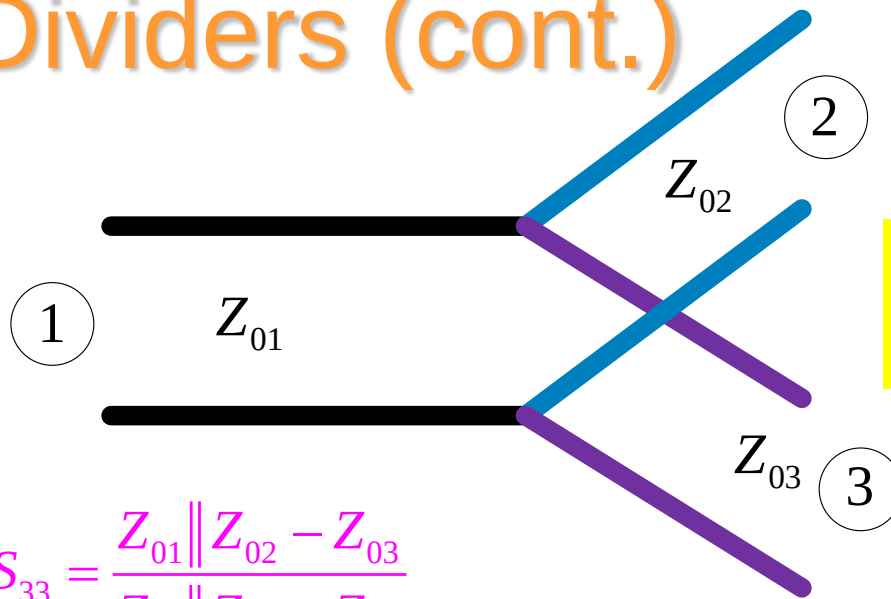
$$S_{32} = S_{23} = (1 + S_{22}) \sqrt{\frac{Z_{02}}{Z_{03}}}$$



$$\frac{P_{\text{out}3}}{P_{\text{out}2}} = \frac{Z_{02}}{Z_{03}}$$

❖ The input port is matched, but not the output ports.



❖ The output ports are not isolated.
❖ Waves reflected from devices on ports 2 and 3 will cause interference with the other devices.

Power Dividers (cont.)

Example: Microstrip T-junction Equal power divider

$$S_{11} = \frac{Z_{02} \parallel Z_{03} - Z_{01}}{Z_{02} \parallel Z_{03} + Z_{01}} = 0$$

$$Z_{02} \parallel Z_{03} = 100 \parallel 100 = 50 \text{ } [\Omega]$$

$$S_{22} = S_{33} = \frac{Z_{01} \parallel Z_{02} - Z_{03}}{Z_{01} \parallel Z_{02} + Z_{03}} = -\frac{1}{2}$$

$$Z_{01} = 50 \text{ } [\Omega]$$

$$Z_{02} = 2Z_{01} = 100 \text{ } [\Omega]$$

$$Z_{01} \parallel Z_{02} = Z_{01} \parallel Z_{03} = 50 \parallel 100 = 33.333 \text{ } [\Omega]$$

$$S_{21} = S_{12} = \sqrt{\frac{Z_{03}}{Z_{02} + Z_{03}}} = \sqrt{\frac{1}{2}}$$

Incident

$$S_{32} = S_{23} = (1 + S_{22}) \sqrt{\frac{Z_{02}}{Z_{03}}} = \frac{1}{2}$$

$$S_{31} = S_{13} = \sqrt{\frac{Z_{02}}{Z_{02} + Z_{03}}} = \sqrt{\frac{1}{2}}$$

For Equal power divider,
 $Z_{02} = Z_{03} = 2Z_{01}$

$$Z_{03} = 2Z_{01} = 100 \text{ } [\Omega]$$

Note: Quarter-wave transformers could be put on the output lines to bring the final output lines back to 50 $[\Omega]$.

Power Dividers (cont.)

The matched power divider also works as a matched power combiner.


$$S_{11} = 0$$

$$S_{22} = S_{33} = -\frac{1}{2}$$

$$S_{21} = S_{12} = \sqrt{\frac{1}{2}}$$

$$S_{31} = S_{13} = \sqrt{\frac{1}{2}}$$

$$S_{32} = S_{23} = \frac{1}{2}$$

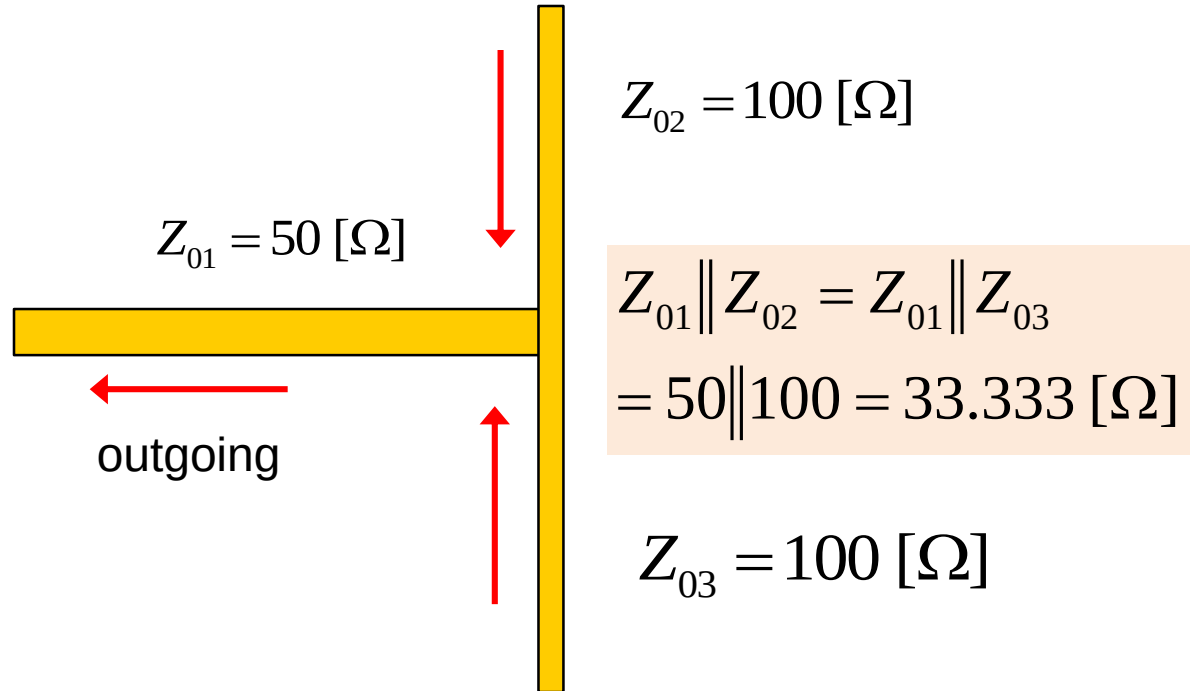

$$b_3 = a_1 S_{31} + a_2 S_{32} + a_3 S_{33}$$

$$= a_3 (S_{33} + S_{32})$$

$$= a_3 \left(-\frac{1}{2} + \frac{1}{2} \right)$$

$$= 0$$

Equal waves are incident from ports 2 and 3 ($a_2 = a_3$).

There is no reflection if equal waves are incident on ports 2 and 3, and port 1 is matched.

EXAMPLE

If source impedance equal to 50 ohm and the power to be divided into 2:1 ratio. Determine Z_1 and Z_2


$$P_{in} = \frac{1}{2} \frac{V_o^2}{Z_o}$$

$$P_1 = \frac{1}{2} \frac{V_o^2}{Z_1} = \frac{1}{3} P_{in} = \frac{1}{2} \frac{1}{3} \frac{V_o^2}{Z_o}$$

$$Z_1 = 3Z_o = 150\Omega$$

$$P_2 = \frac{1}{2} \frac{V_o^2}{Z_2} = \frac{1}{2} \frac{2}{3} \frac{V_o^2}{Z_o} P_{in}$$

$$Z_2 = \frac{3Z_o}{2} = 75\Omega$$

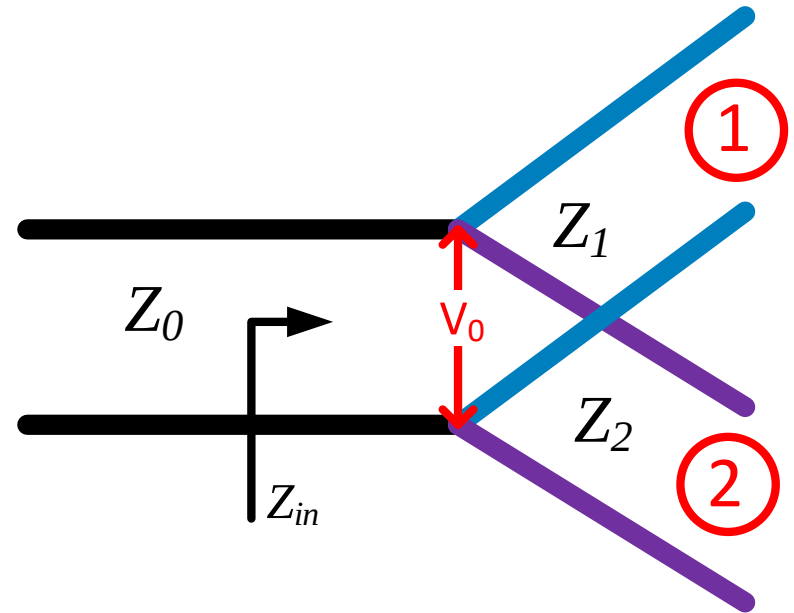


$$Z_{in} = Z_1 // Z_2 = 50\Omega = Z_o$$

RESISTIVE DIVIDER

- If a three-port divider contains lossy components, it can be made to be matched at all ports, although the two output ports may not be isolated.
- An equal-split (-3 dB) divider is shown in Figure, using lumped-element resistors, but unequal power division ratios are also possible.
- Assuming that all ports are terminated in the characteristic impedance Z_0 .

RESISTIVE DIVIDER

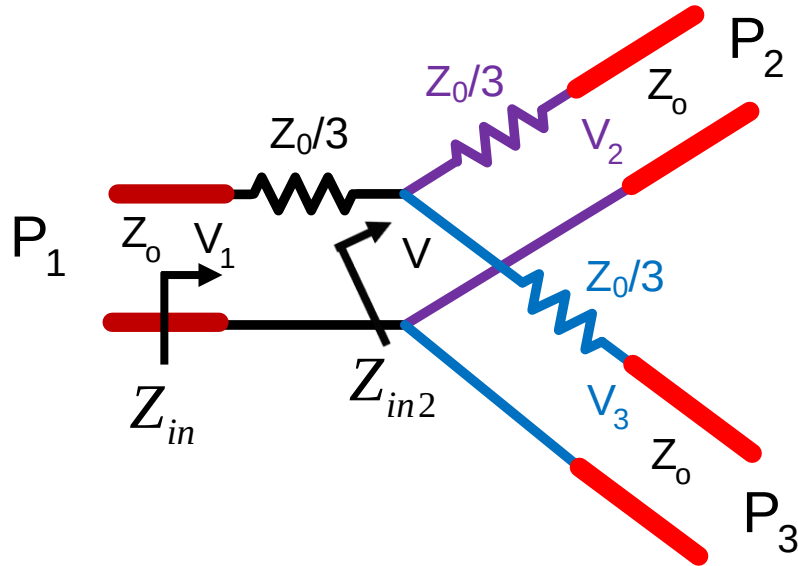

$$Z_{in2} = Z_o + \frac{Z_o}{3} = \frac{4Z_o}{3} = Z_{in3}$$

Then the input impedance of the divider is

$$Z_{in} = \frac{Z_o}{3} + \frac{4Z_o}{3} \parallel \frac{4Z_o}{3} = \frac{Z_o}{3} + \frac{2Z_o}{3} = Z_o$$

$$V = \frac{2Z_o / 3}{Z_o / 3 + 2Z_o / 3} V_1 = \frac{2}{3} V_1$$

$$V_2 = V_3 = \frac{Z_o}{Z_o + Z_o / 3} V = \frac{3}{4} V = \frac{1}{2} V_1$$

$$P_{in} = \frac{1}{2} \frac{V_1^2}{Z_o}$$

$$P_2 = P_3 = \frac{1}{2} \frac{(1/2 V_1)^2}{Z_o} = \frac{1}{4} P_{in}$$

RESISTIVE DIVIDER

$$\text{Power loss} = P_{\text{Loss}} = P_{\text{in}} - (P_2 + P_3) = P_{\text{in}} - \frac{1}{2} P_{\text{in}} = \frac{1}{2} P_{\text{in}}$$

- ❖ Thus, $S_{21} = S_{31} = S_{23} = 1/2$, which is -6 dB below the input power level.
- ❖ The network is reciprocal, so the scattering matrix is symmetric, and can be written as

$$[S] = \frac{1}{2} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix}$$


THE WILKINSON POWER DIVIDER

- ❖ The lossless T-junction divider suffers from the problem of not being matched at all port.
- ❖ The lossless T-junction divider does not have any isolation between output ports.
- ❖ The resistive divider can be matched at all ports, but even though it is not lossless, isolation is still not achieved.

THE WILKINSON POWER DIVIDER

- ❖ We know that a lossy three-port network can be made having all ports matched with isolation between the output.
- ❖ The Wilkinson power divider is such a network, with the useful property of being lossless when the output ports are matched.
- ❖ In the Wilkinson power divider, only reflected power from two out ports is dissipated.

THE WILKINSON POWER DIVIDER

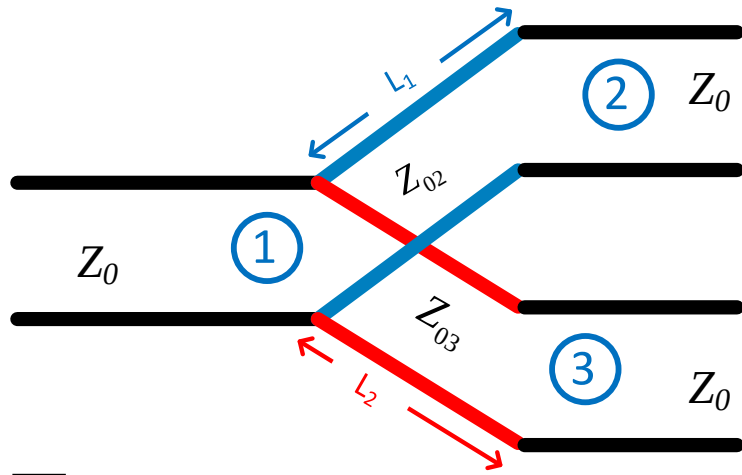


$$L_1 = L_2 = \lambda_g / 4$$

$$Z_{02} = Z_{03} = \sqrt{2}Z_0$$

❖ Two output are not Matched

❖ Two output are not isolated

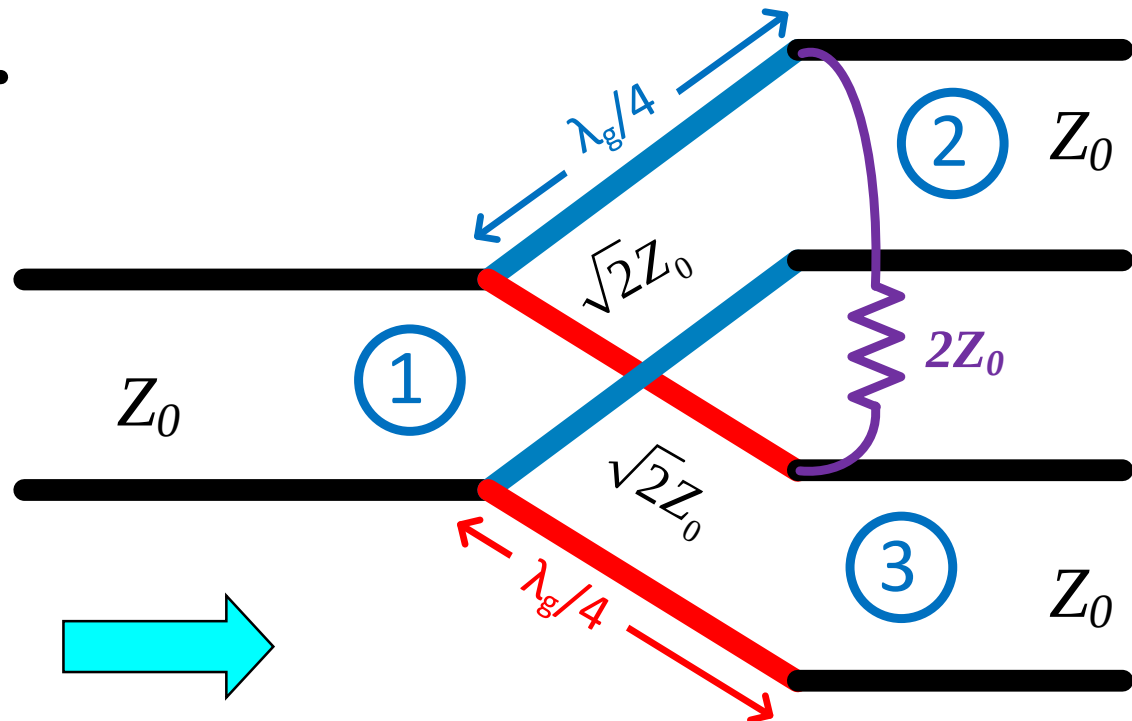

❖ For isolation between output, $2Z_0$ are added

Wilkinson Power Divider


Equal-split (3 dB) power divider

(The Wilkinson can also be designed to have an unequal split.)

- ❖ All ports matched ($S_{11} = S_{22} = S_{33} = 0$)
- ❖ Output ports are isolated ($S_{23} = S_{32} = 0$)

Note: No power is lost in going from port 1 to ports 2 and 3:

$$|S_{21}|^2 = |S_{31}|^2 = \frac{1}{2}$$

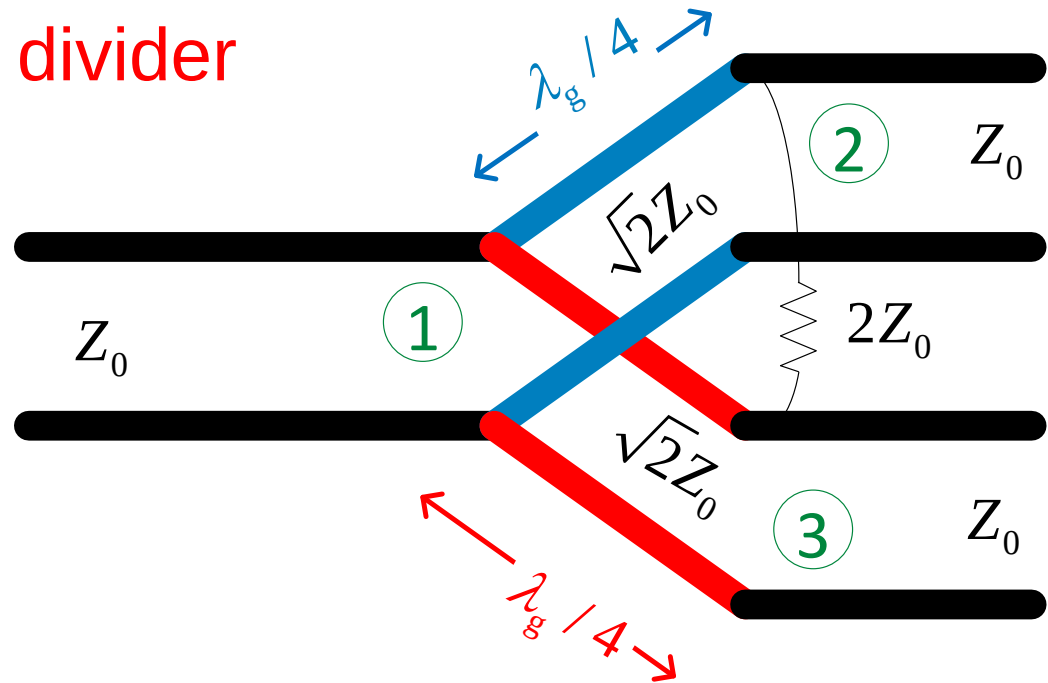

$$[S] = \frac{-j}{\sqrt{2}} \begin{pmatrix} 0 & 1 & 1 \\ 1 & 0 & 0 \\ 1 & 0 & 0 \end{pmatrix}$$


Obviously not unitary

Wilkinson Power Divider (cont.)

$$[S] = \frac{-j}{\sqrt{2}} \begin{pmatrix} 0 & 1 & 1 \\ 1 & 0 & 0 \\ 1 & 0 & 0 \end{pmatrix}$$



Microstrip layout

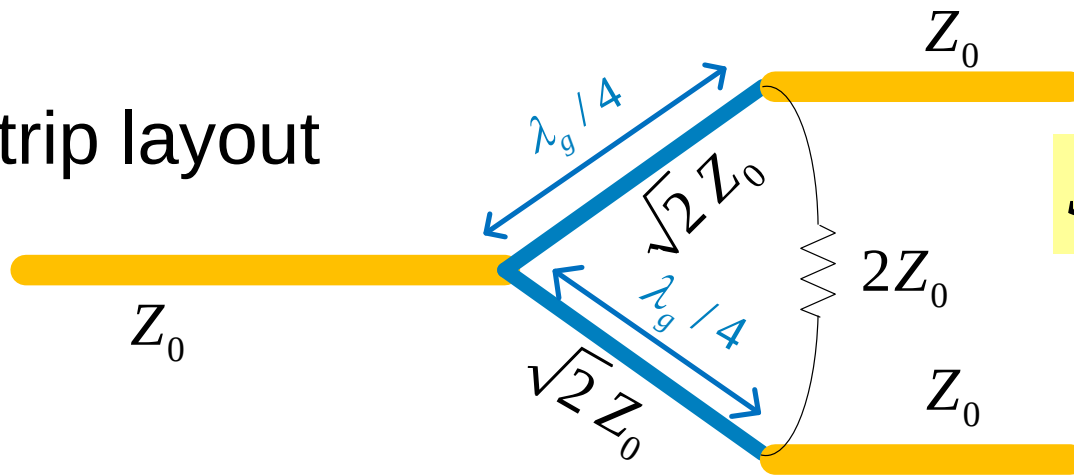


$$S_{11} = S_{22} = S_{33} = 0$$

$$S_{32} = S_{23} = 0$$

All three ports are matched, and the output ports are isolated.

Wilkinson Power Divider (cont.)
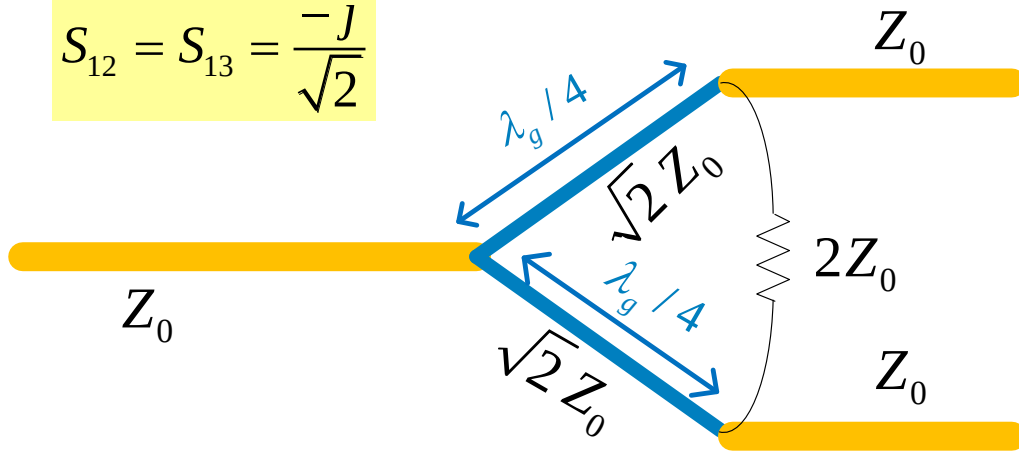
$$S_{12} = S_{13} = \frac{-j}{\sqrt{2}}$$




$$[S] = \frac{-j}{\sqrt{2}} \begin{pmatrix} 0 & 1 & 1 \\ 1 & 0 & 0 \\ 1 & 0 & 0 \end{pmatrix}$$

$$S_{21} = S_{31} = \frac{-j}{\sqrt{2}}$$

- ❖ When a wave is incident from port 1, half of the total incident power gets transmitted to each output port (no loss of power).
- ❖ When a wave is incident from port 2 or port 3, half of the power gets transmitted to port 1 and half gets absorbed by the resistor.
- ❖ But nothing gets through to the other output port (the two output ports are isolated from each other).


Wilkinson Power Divider (cont.)

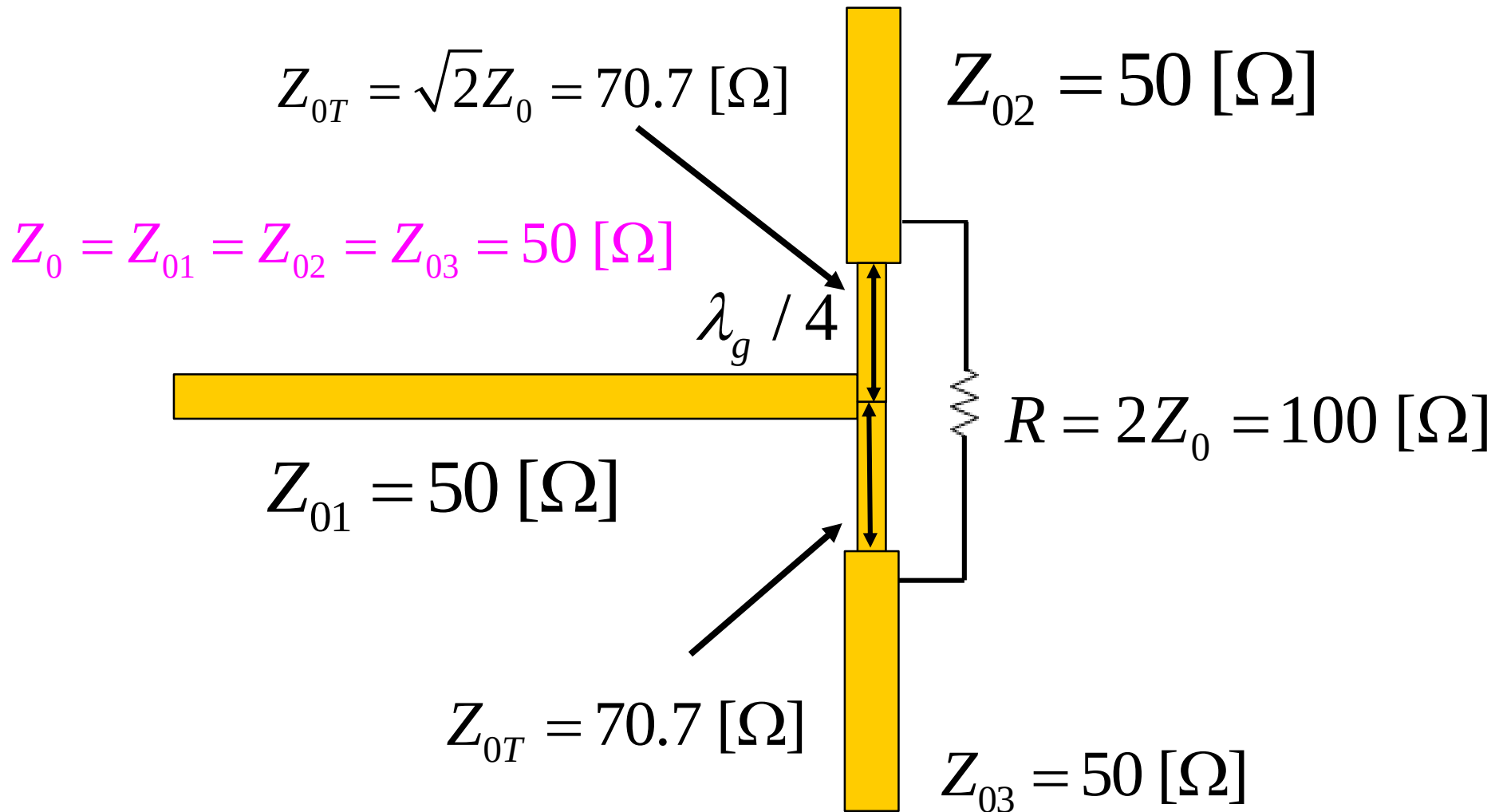Example: Microstrip Wilkinson power divider




Wilkinson Power Divider (cont.)

Figure 7.15 of Pozar
Photograph of a four-
way corporate power
divider network using
three microstrip
Wilkinson power
dividers. Note the
isolation chip resistors.

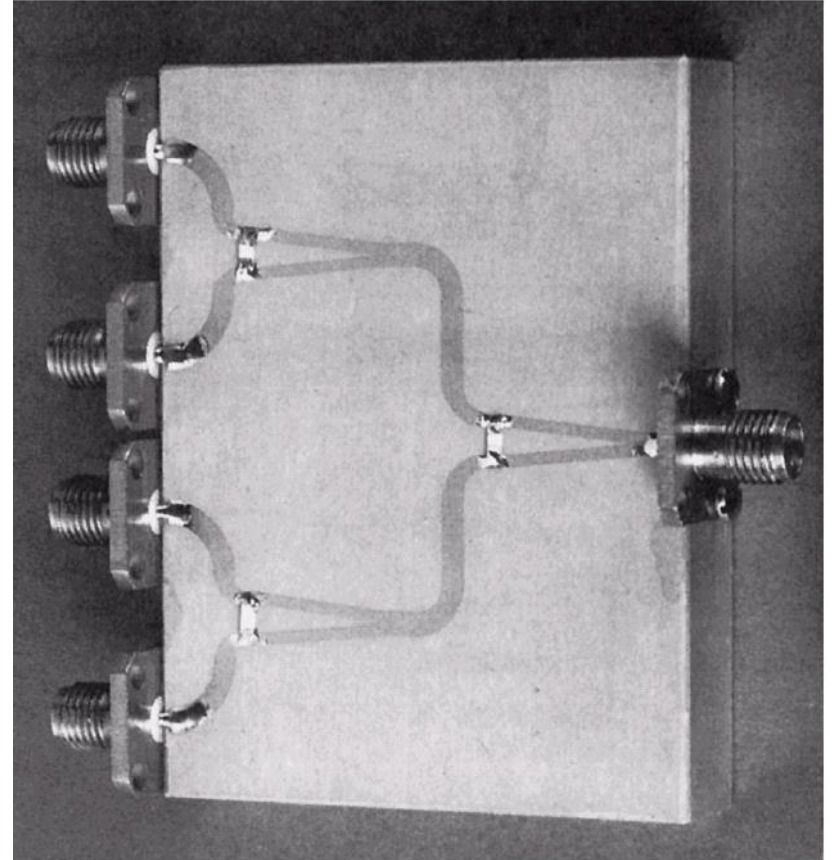

Wilkinson Power Divider

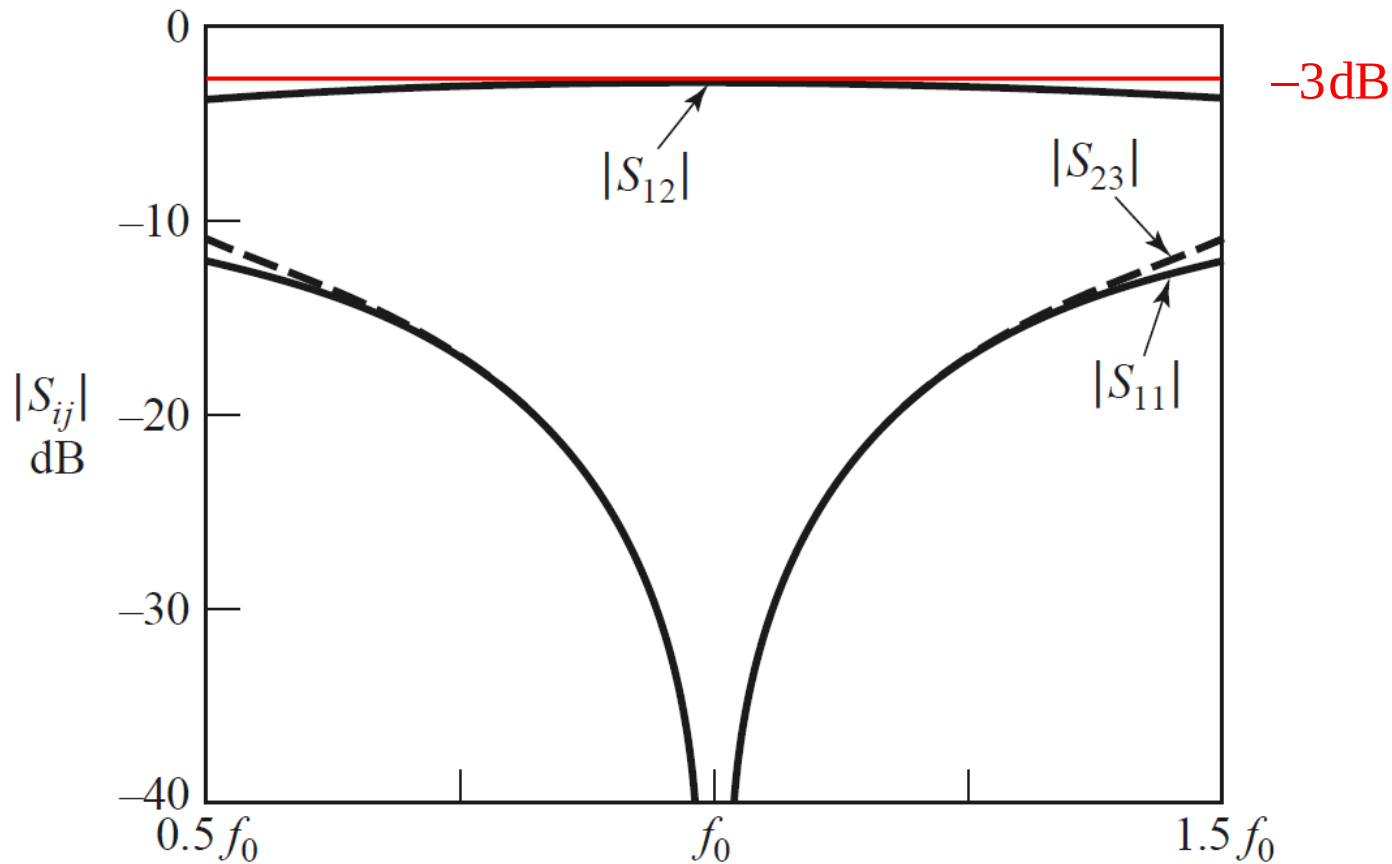

- ❖ Figure depict Frequency response of an equal-split Wilkinson power divider.
- ❖ Port 1 is the input port; ports 2 and 3 are the output ports.

ODD AND EVEN MODE ANALYSIS

Usually use for analyzing a symmetrical four port network

(1) Excitation: ➤ Equal ,in phase excitation → even mode
➤ Equal ,out of phase excitation → odd mode

(2) Draw intersection line for symmetry and apply

- ❖ short circuit for odd mode
- ❖ Open circuit for even mode

(3) Also can apply EM analysis of the structure

- ❑ Tangential E field zero – odd mode
- ❑ Tangential H field zero – even mode

(4) Single excitation at one port = even mode + odd mode

Wilkinson Power Divider (cont.)

The analysis of the Wilkinson power divider is given here.

- ❖ Even/odd mode analysis is used to analyze the Wilkinson power divider.
- ❖ This requires two separate analyzes (even and odd).
- ❖ Each analysis involves only a two-port device instead of a three-port device.

Wilkinson Power Divider (cont.)

- ❖ Even and odd analysis is used to analyze the structure when **port 2** is excited.


⇒ To determine S_{22} , S_{32}

- ❖ Only even analysis is needed to analyze the structure when **port 1** is excited.

⇒ To determine S_{11} , S_{21}

- ❖ The other five components of the S matrix can be found by using physical symmetry and reciprocity (the symmetry of the S matrix).

Wilkinson Power Divider (cont.)

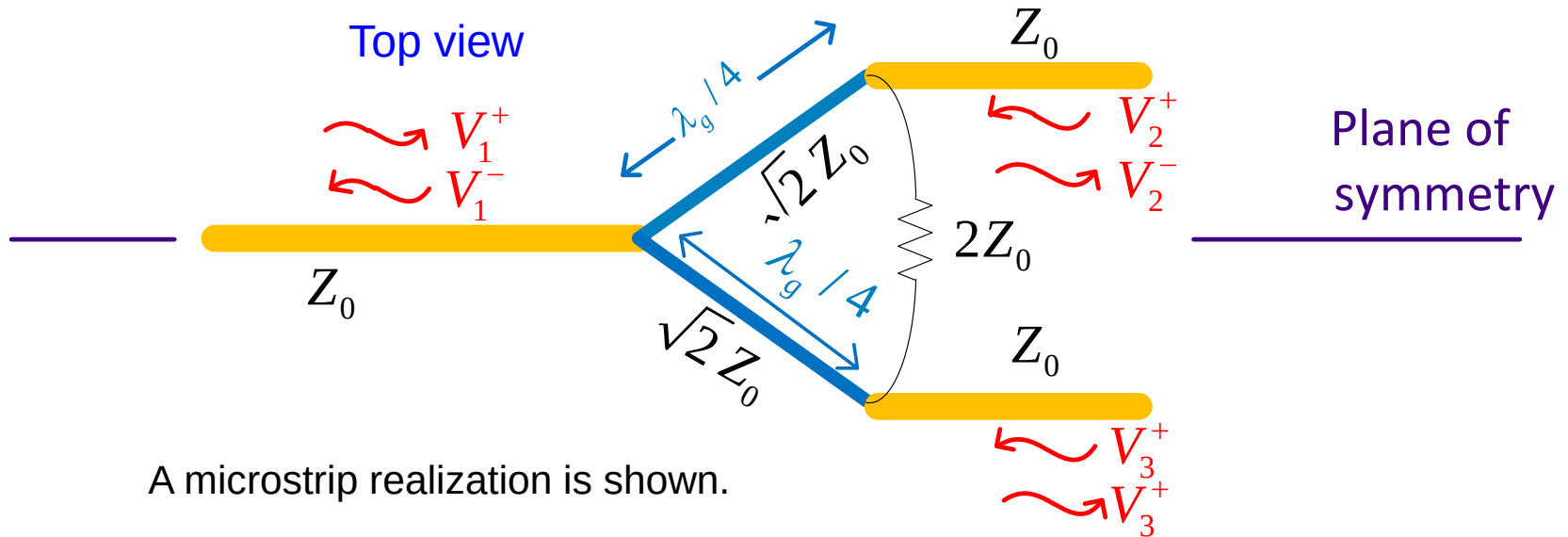


Split structure along plane of symmetry (POS)

Even $\Rightarrow$ voltage even about POS $\Rightarrow$ place OC along POS


Odd $\Rightarrow$ voltage odd about POS $\Rightarrow$ place SC along POS

Wilkinson Power Divider (cont.)

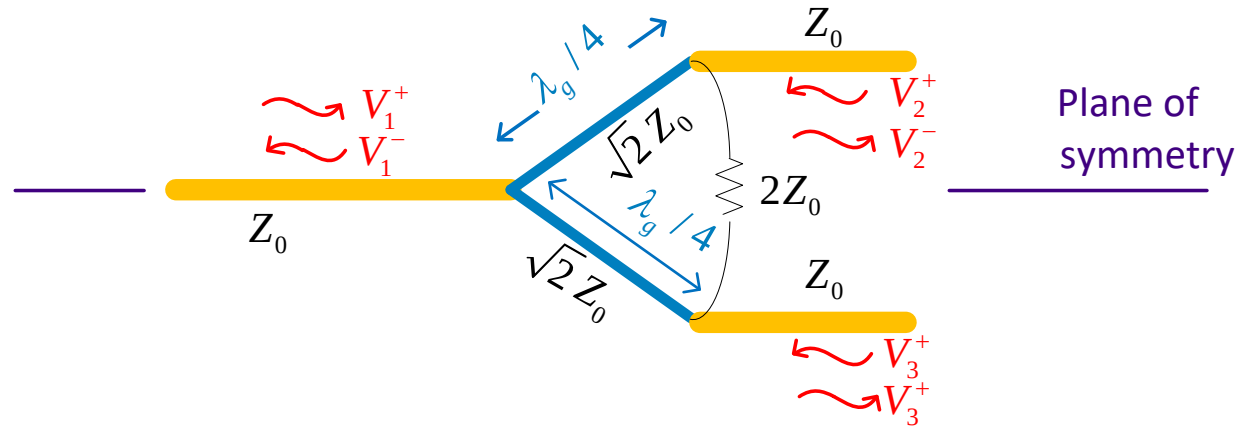

How do you split a transmission line? (This is needed for the even case.)

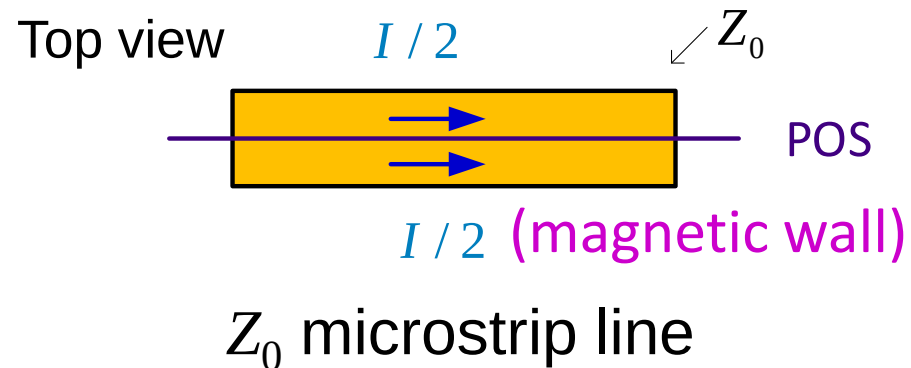- ❖ Voltage is the same for each half of line (V)
- ❖ Current is halved for each half of line ($I/2$)




For each half $\Rightarrow Z_0^h = \frac{V}{I/2} = 2Z_0$

Wilkinson Power Divider (cont.)


Port 2 Excitation
“even” problem

Overview

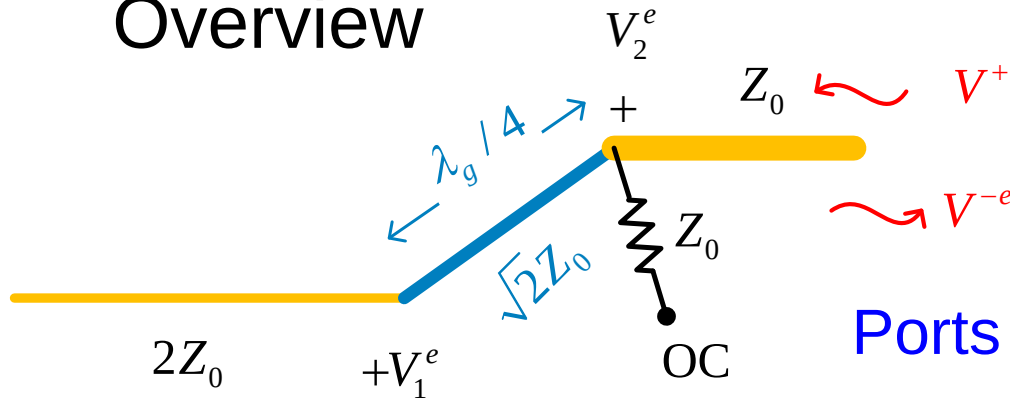

Note:
The $2Z_0$ resistor has been split into two Z_0 resistors in series.

Ports 2 and 3 are excited in phase.

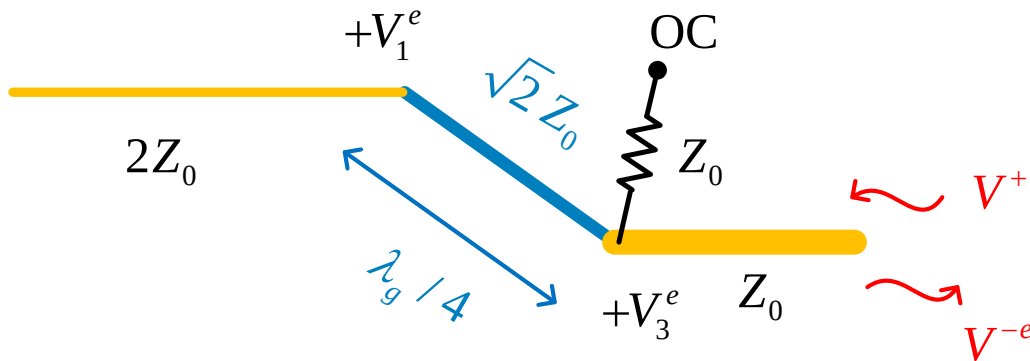

Note: $V_3^e = V_2^e$

$$\Rightarrow S_{22}^e, S_{32}^e$$


$$S_{22}^e \equiv \frac{V^{-e}}{V^{+}}$$

$$S_{32}^e \equiv \frac{V^{-e}}{V^{+}} = S_{22}^e$$


Wilkinson Power Divider (cont.)

Port 2 Excitation “odd” problem

Overview

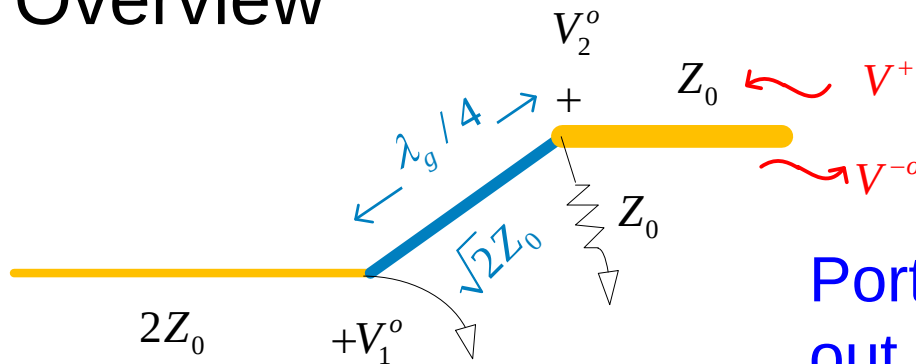

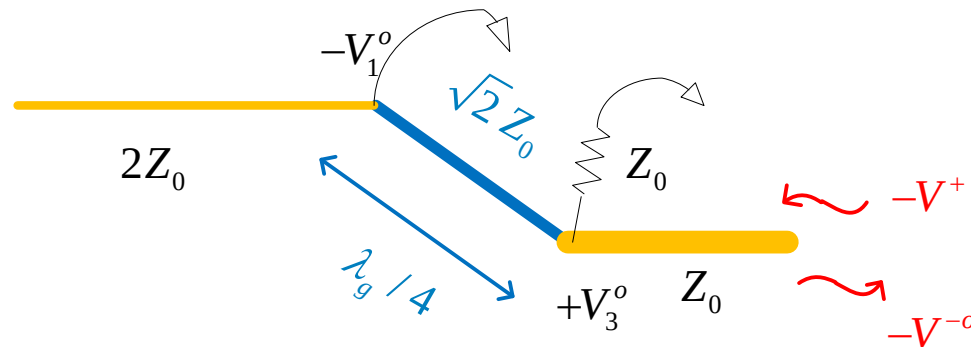Ports 2 and 3 are excited 180° out of phase.



Note: $V_1^o = 0$, $V_3^o = -V_2^o$

Note:

The $2Z_0$ resistor has been split into two Z_0 resistors in series.

$$\Rightarrow S_{22}^o, S_{32}^o$$

$$S_{22}^o \equiv \frac{V^{-o}}{V^+}$$

$$S_{32}^o \equiv \frac{-V^{-o}}{V^+} = -S_{22}^o$$

Wilkinson Power Divider (cont.)


Port 2 Excitation

“even” problem (Analysis)

$$Z_{\text{in}2}^e = \frac{Z_T^2}{Z_L}$$

$$Z_{\text{in}2}^e = \frac{(\sqrt{2} Z_0)^2}{2Z_0} = Z_0$$
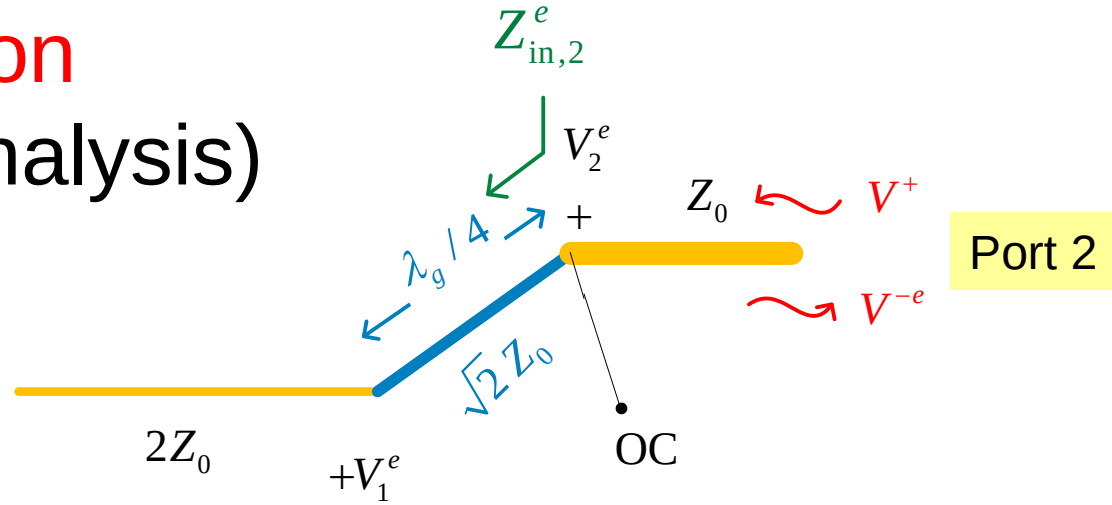
$$\Rightarrow S_{22}^e = \frac{Z_{\text{in}2}^e - Z_0}{Z_{\text{in}2}^e + Z_0} = 0$$



(quarter-wave transformer)

Also, by physical symmetry:

$$S_{33}^e = S_{22}^e = 0$$

Also, in the even case: $S_{32}^e = S_{22}^e \Rightarrow S_{32}^e = 0$

Wilkinson Power Divider (cont.)

Port 2 Excitation


“odd” problem (Analysis)

$$Z_{in2}^o = \frac{Z_T^2}{Z_L}$$

$$= \frac{(\sqrt{2} Z_0)^2}{0} = \infty$$

$$Z_{in2}^o = \infty \parallel Z_0 = Z_0$$
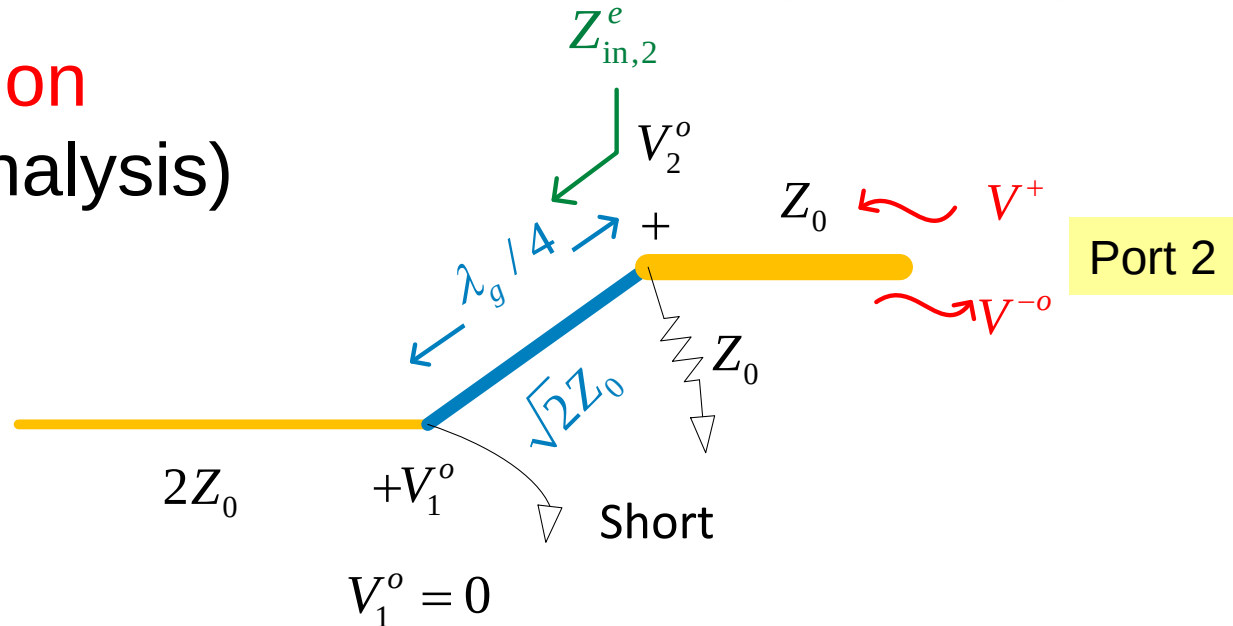
$$\Rightarrow S_{22}^o = \frac{Z_{in2}^o - Z_0}{Z_{in2}^o + Z_0} = 0$$



Also, by physical symmetry:

$$S_{33}^o = S_{22}^o = 0$$

Also, in the odd case:

$$S_{32}^o = -S_{22}^o \Rightarrow S_{32}^o = 0$$

Wilkinson Power Divider (cont.)

We now add the results from the even and odd cases together:

$$S_{22} = \left. \frac{V_2^-}{V_2^+} \right|_{a_1=a_3=0} = \frac{V^{-e} + V^{-o}}{V^+ + V^+} = \frac{V^{-e} + V^{-o}}{2V^+} = \frac{1}{2}(S_{22}^e + S_{22}^o) = \frac{1}{2}(0 + 0) = 0$$

$$\Rightarrow S_{33} = 0 \quad (\text{by symmetry})$$

$$S_{32} = \left. \frac{V_3^-}{V_2^+} \right|_{a_1=a_3=0} = \frac{V^{-e} - V^{-o}}{V^+ + V^+} = \frac{V^{-e} - V^{-o}}{2V^+} = \frac{1}{2}(S_{32}^e - S_{32}^o) = \frac{1}{2}(0 - 0) = 0$$

$$\Rightarrow S_{23} = 0 \quad (\text{by reciprocity})$$

In summary, for port 2 excitation, we have:

Note: Since all ports have the same Z_0 , we ignore the normalizing factor $\sqrt{Z_0}$ in the S parameter definition.

$$S_{22} = 0$$


$$S_{33} = 0$$

$$S_{32} = S_{23} = 0$$

Wilkinson Power Divider (cont.)

Port 1 Excitation

“even” problem Overview

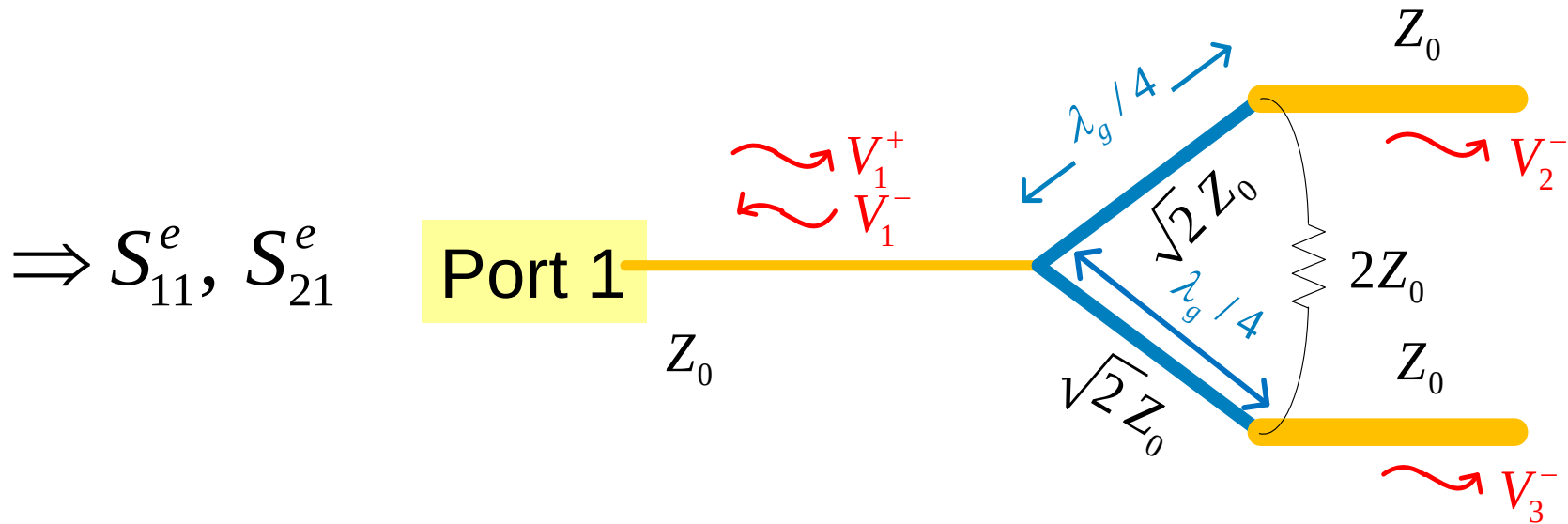

When port 1 is excited, the response, by symmetry, is even.


(Hence, the total voltages are the same as the even voltages.)

Wilkinson Power Divider (cont.)

Port 1 Excitation


“even” problem (Analysis)

Top view

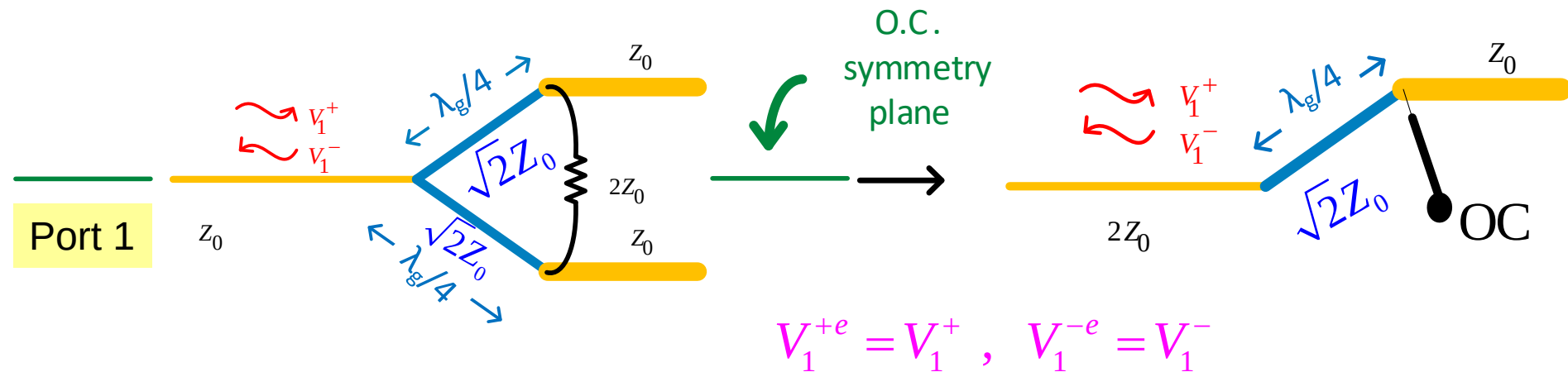

$$I_1^e = I_1 / 2$$

$$V_1^e = V_1$$

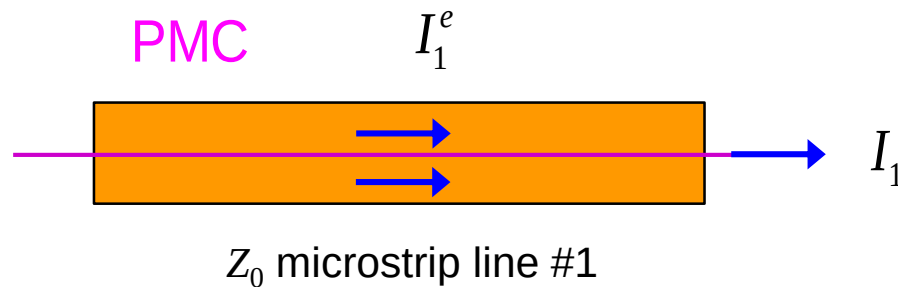

Wilkinson Power Divider (cont.)


Port 1 Excitation
“even” problem

Analysis (cont.)

$$Z_{in1}^e = \frac{(\sqrt{2}Z_0)^2}{Z_0} = 2Z_0$$

$$S_{11}^e = \frac{Z_{in1}^e - 2Z_0}{Z_{in1}^e + 2Z_0} = 0$$

$$S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{a_2=a_3=0} = \left. \frac{V_1^{-e}}{V_1^{+e}} \right|_{a_2=0} = S_{11}^e = 0$$

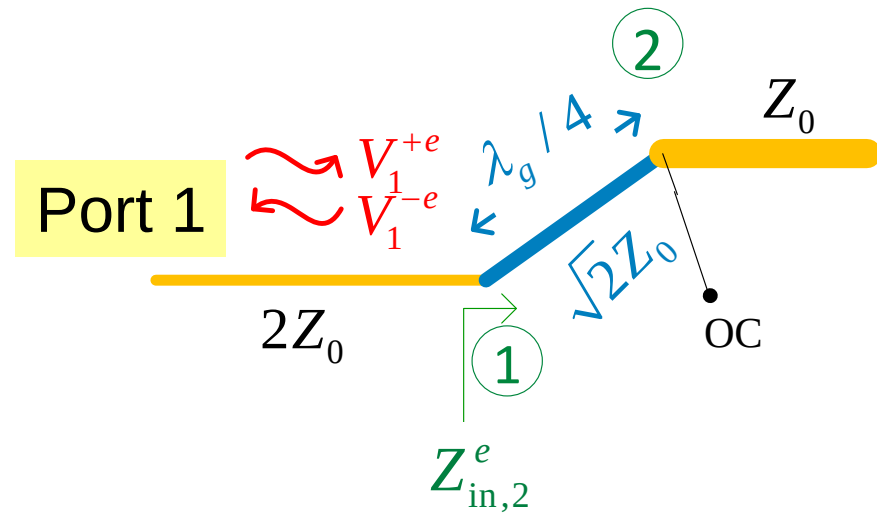

Recall:

$$Z_{in} = \frac{Z_T^2}{Z_L}$$

(quarter-wave transformer)

Hence

$$S_{11} = 0$$

Wilkinson Power Divider (cont.)


Port 1 Excitation
“even” problem
Analysis (cont.)

$$S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{a_2=a_3=0} = \left. \frac{V_2^-}{V_1^+} \right|_{a_2=a_3=0} = S_{21}^e$$

$$V_2^{-e} = V_2^e$$


$$V_1^e = V_1^{+e} (1 + S_{11}^e) = V_1^{+e}$$
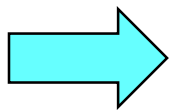
$$\Rightarrow S_{21}^e = \frac{V_2^-}{V_1^+} = \frac{V_2^e}{V_1^e} = -j \frac{(1+\Gamma)}{(1-\Gamma)} = -j \frac{2}{2\sqrt{2}}$$



$$S_{21} = \frac{-j}{\sqrt{2}} = S_{12}$$

(symmetry of S matrix)

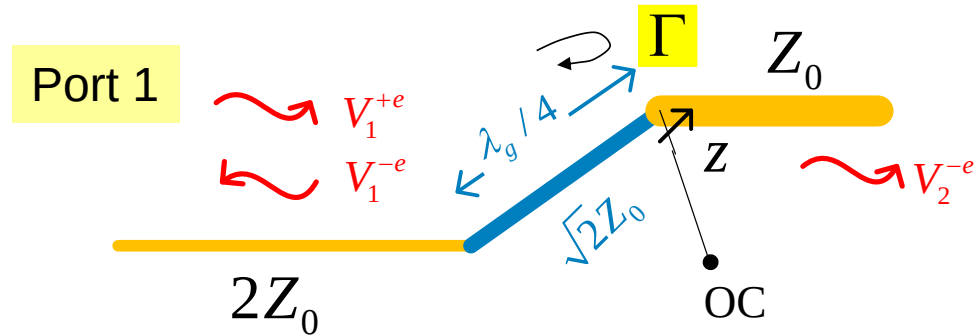

Along $\lambda_g/4$ wave transformer:

$$V_T^e(z) = V_0^+ e^{-j\beta z} (1 + \Gamma e^{+j2\beta z})$$

z = distance from port 2

$$\left\{ \begin{array}{l} V_2^e = V_T^e(0) = V_0^+ (1 + \Gamma) \\ V_1^e = V_T^e(-\lambda_g/4) = V_0^+ j(1 - \Gamma) \end{array} \right.$$

$$\Gamma = \frac{Z_0 - \sqrt{2}Z_0}{Z_0 + \sqrt{2}Z_0} = \frac{1 - \sqrt{2}}{1 + \sqrt{2}}$$

$$1 + \Gamma = \frac{2}{1 + \sqrt{2}} \quad 1 - \Gamma = \frac{2\sqrt{2}}{1 + \sqrt{2}}$$

Wilkinson Power Divider (cont.)

For the other two components:

By physical symmetry: $S_{31} = S_{21} = \frac{-j}{\sqrt{2}}$

By reciprocity (symmetry of S matrix):


$$S_{13} = S_{31} = \frac{-j}{\sqrt{2}}$$

We then have the final S matrix:

$$[S] = \frac{-j}{\sqrt{2}} \begin{pmatrix} 0 & 1 & 1 \\ 1 & 0 & 0 \\ 1 & 0 & 0 \end{pmatrix}$$

UNEQUAL POWER DIVISION AND N-WAY WILKINSON DIVIDERS

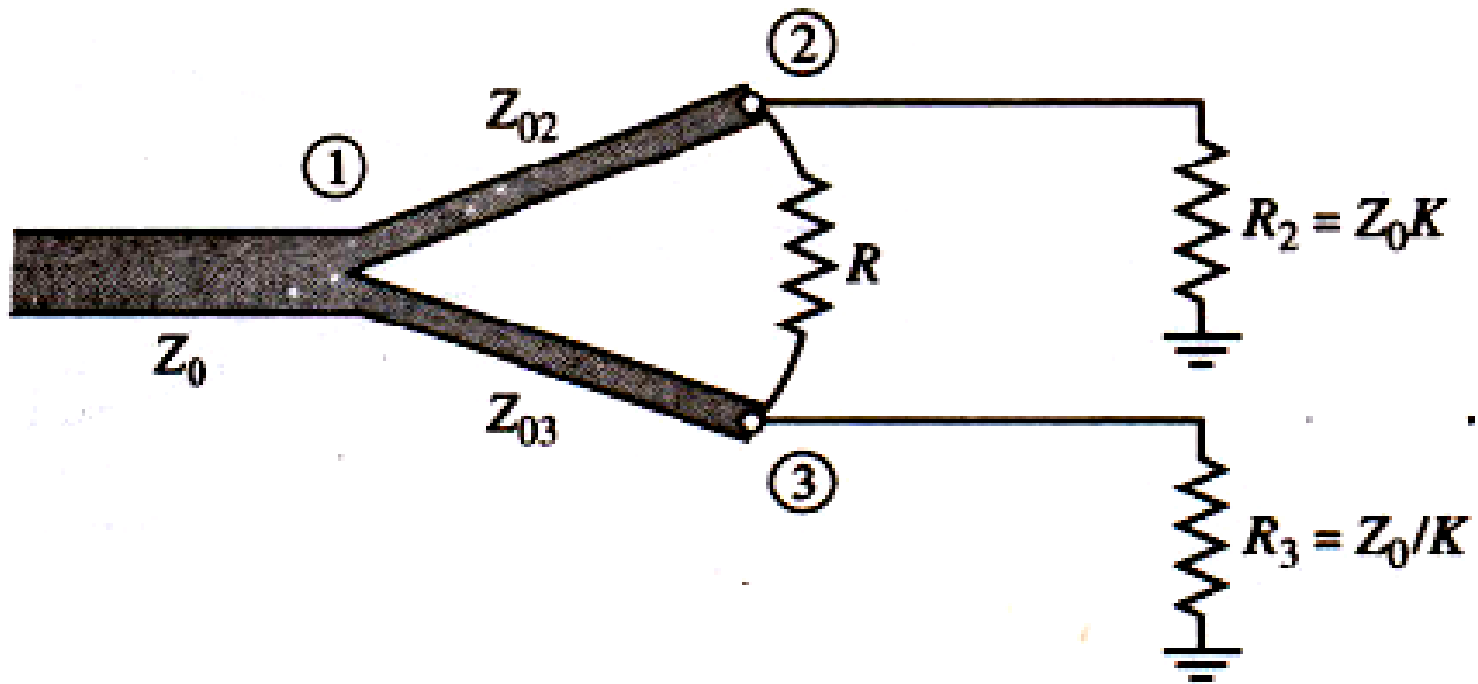Wilkinson-type power dividers can also be made with unequal power splits; a microstrip version is shown in Figure 7.13. If the power ratio between ports 2 and 3 is $K^2 = P_3/P_1$



then the following design equations apply:


$$Z_{03} = Z_0 \sqrt{\frac{1 + K^2}{K^3}},$$

$$Z_{02} = K^2 Z_{03} = Z_0 \sqrt{K(1 + K^2)},$$

$$R = Z_0 \left(K + \frac{1}{K} \right).$$

$$R_2 = Z_0 K \quad \text{and} \quad R_3 = Z_0 / K$$

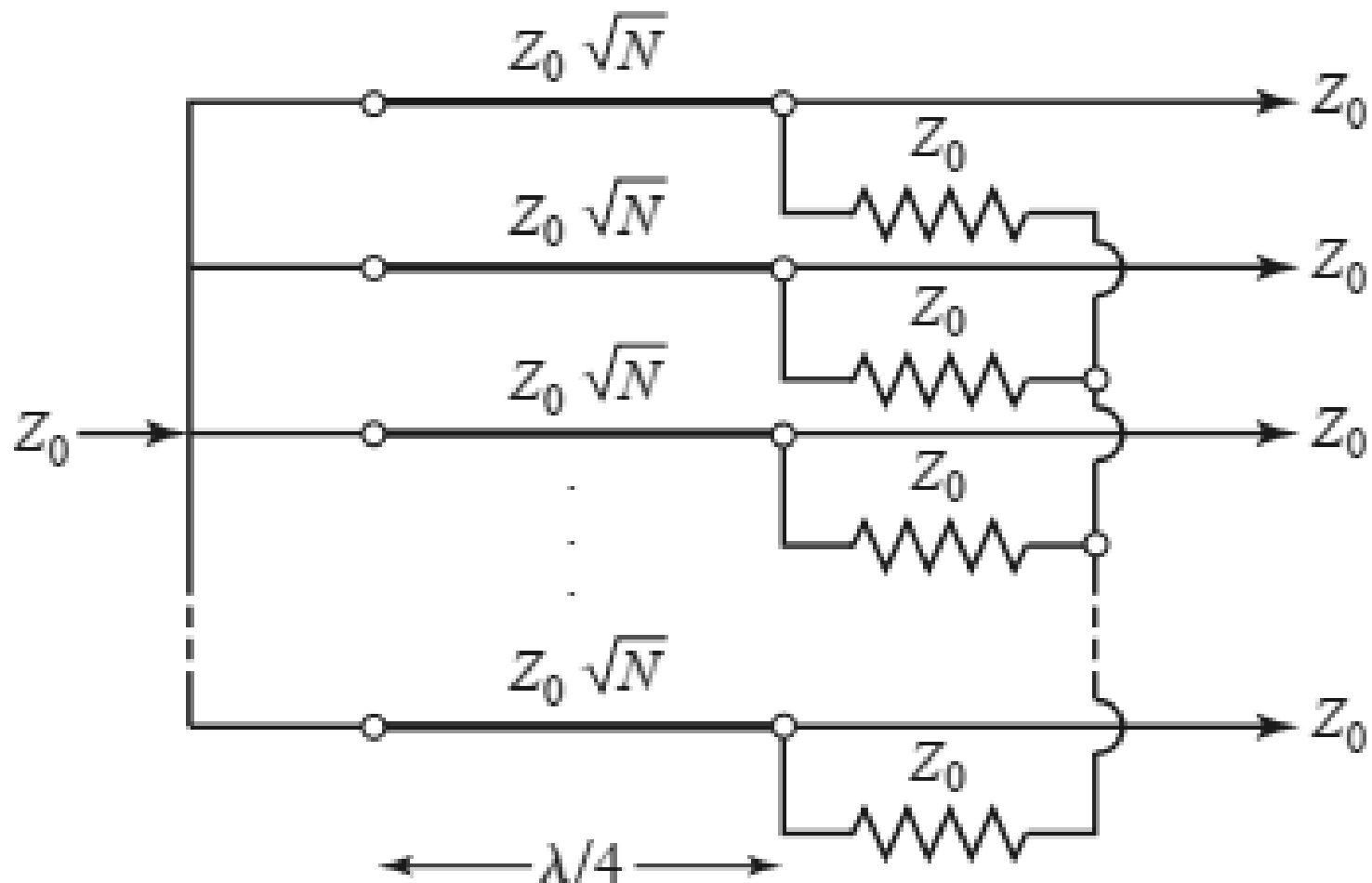AN N -WAY, EQUAL-SPLIT WILKINSON POWER DIVIDER.



EXAMPLE

Design an equal-split Wilkinson power divider for a 50 W system impedance at frequency f_0


The quarterwave-transformer characteristic is

$$Z = \sqrt{2} Z_0 = 70.7\Omega$$

$$R = 2Z_0 = 100\Omega$$

The quarterwave-transformer length is $\ell = \frac{\lambda_0}{4\sqrt{\epsilon_r}}$

UNEQUAL POWER WILKINSON DIVIDER

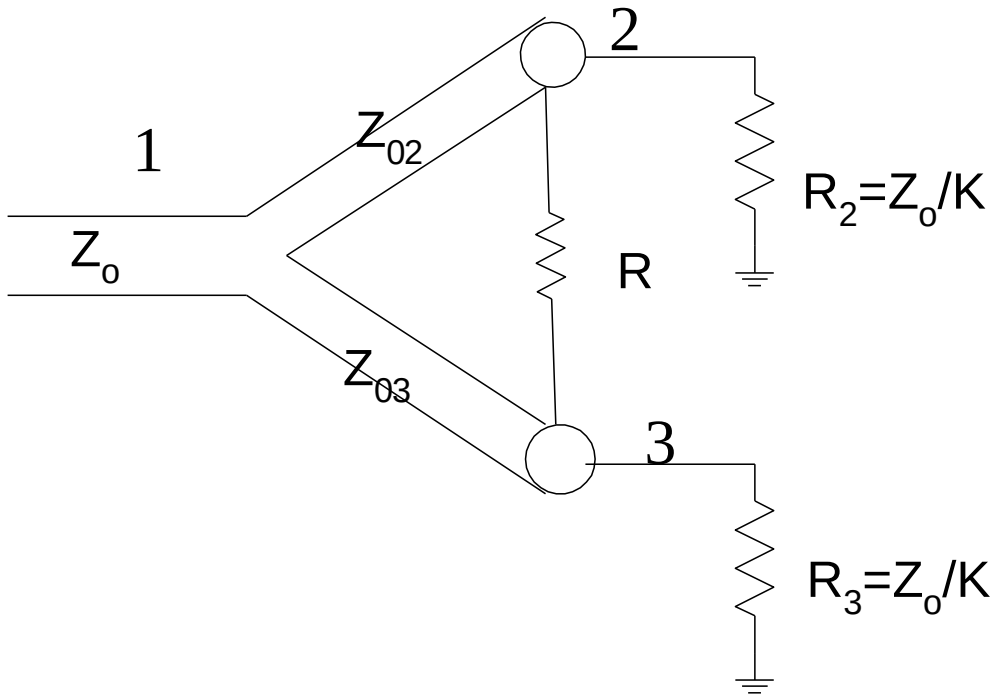

$$Z_{03} = Z_0 \sqrt{\frac{1 + K^2}{K^3}}$$

$$Z_{02} = K^2 Z_{03} = Z_0 \sqrt{K(1 + K^2)}$$

$$R = Z_0 \left(K + \frac{1}{K} \right)$$

$$K^2 = \frac{P_3}{P_2} = \frac{\text{Power at port - 3}}{\text{Power at port - 2}}$$

Circulators

Now consider a 3-port network that is **non-reciprocal**, with all ports matched, and is lossless:

$$\Rightarrow [S] = \begin{pmatrix} 0 & S_{12} & S_{13} \\ S_{21} & 0 & S_{23} \\ S_{31} & S_{32} & 0 \end{pmatrix}$$

$$S_{ij} \neq S_{ji}$$

“Circulator”



These equations will be satisfied if:

(There are six distinct values.)

Lossless $\Rightarrow |S_{21}|^2 + |S_{31}|^2 = 1$
(unitary) $|S_{12}|^2 + |S_{32}|^2 = 1$
 $|S_{13}|^2 + |S_{23}|^2 = 1$
 $S_{31} S_{32}^* = 0$
 $S_{21} S_{23}^* = 0$
 $S_{12} S_{13}^* = 0$

①

$$S_{12} = S_{23} = S_{31} = 0$$

$$|S_{21}| = |S_{32}| = |S_{13}| = 1$$

or

②

$$S_{21} = S_{32} = S_{13} = 0$$

$$|S_{12}| = |S_{23}| = |S_{31}| = 1$$

Circulators (cont.)



① $[S] = \begin{pmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{pmatrix}$

Note: We have assumed here that the phases of all the S parameters are zero.

② $[S] = \begin{pmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \end{pmatrix}$

A wave goes in one port and comes out from the adjacent port!

Clockwise (LH) circulator

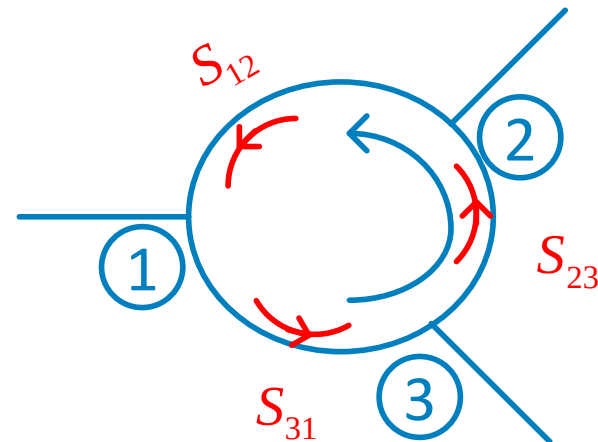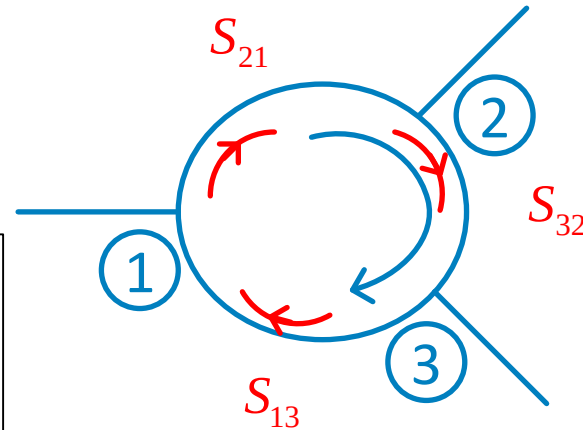

Counter-clockwise (RH) circulator

Circulators (cont.)

An example of a circulator:



Frequency: 0.698 – 0.96 GHz

VSWR: <1.3

Isolation : >18 dB

Power: 1000 W

Insertion loss: <0.35 dB

Length: 1.75 in

Width: 2 in

Height: 1.02 in


Temperature range: -20 – 70 deg C

Price: \$439.94

Circulators can be made using biased ferrite materials.

Circulators (cont.)

Application: Wireless system

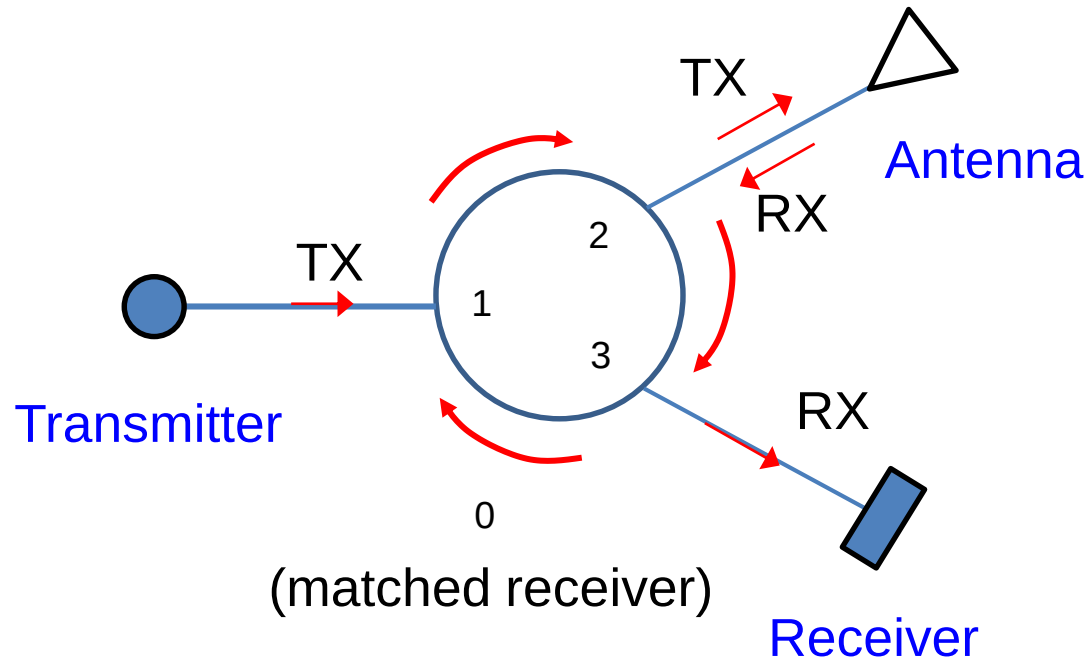

- ❖ The same antenna can be used for transmit and receive.
- ❖ The transmit and receive frequencies can even be the same.

Note: A circulator used this way is often called a duplexer.


Duplexer

A duplexer:



Diplexer

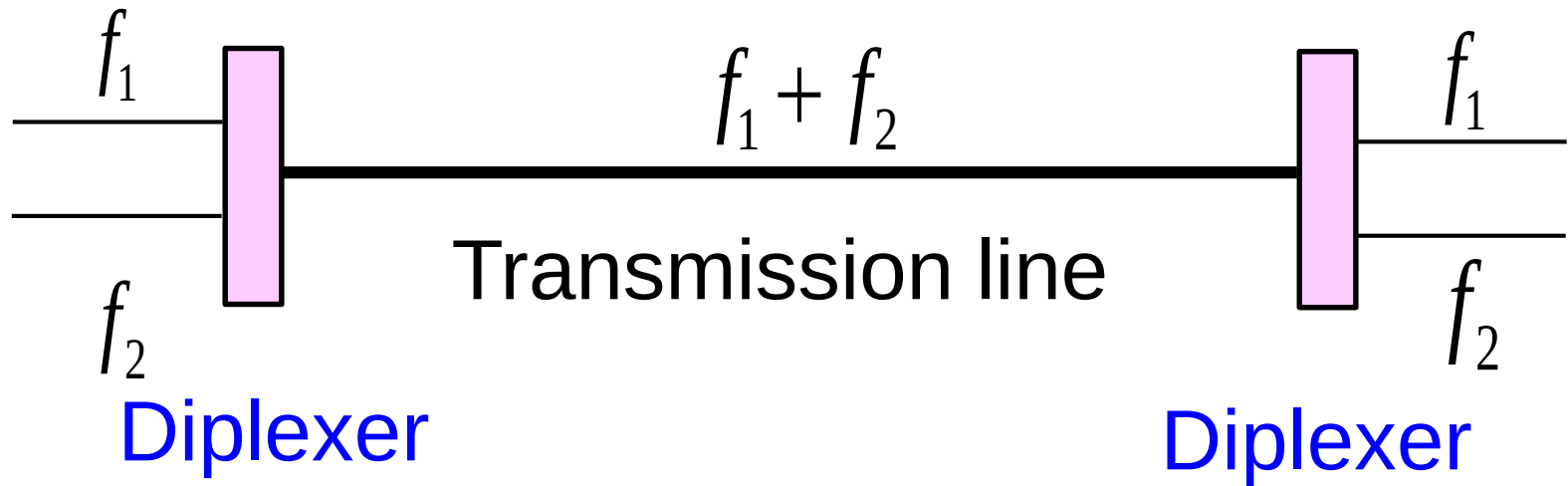A diplexer is a type of filter that combines or splits two different frequencies (f_1 and f_2).




Triplexer: three frequencies

Multiplexer: multiple frequencies


Diplexer (cont.)

An example of a diplexer:

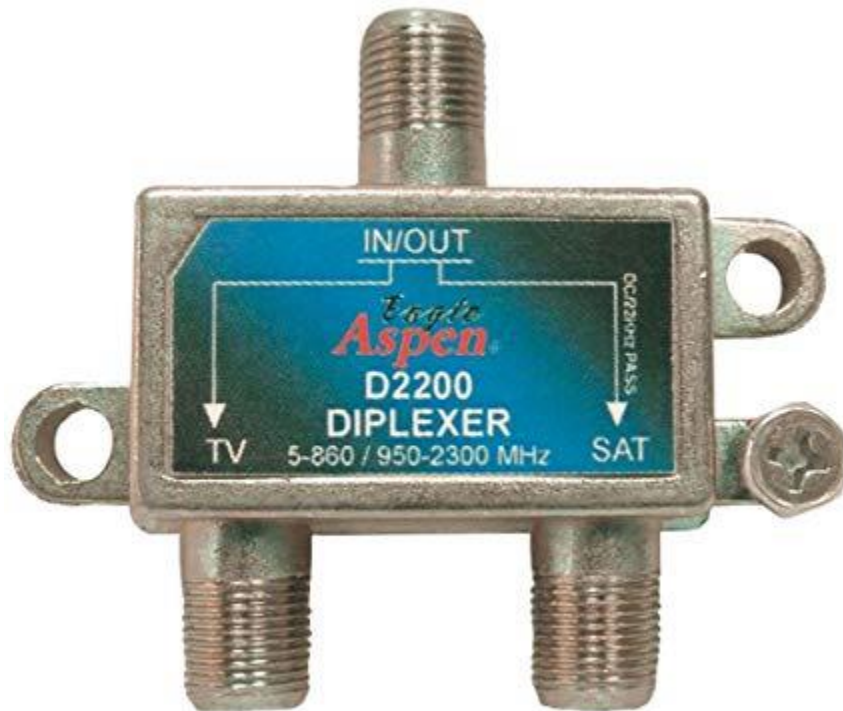

Diplexer (cont.)

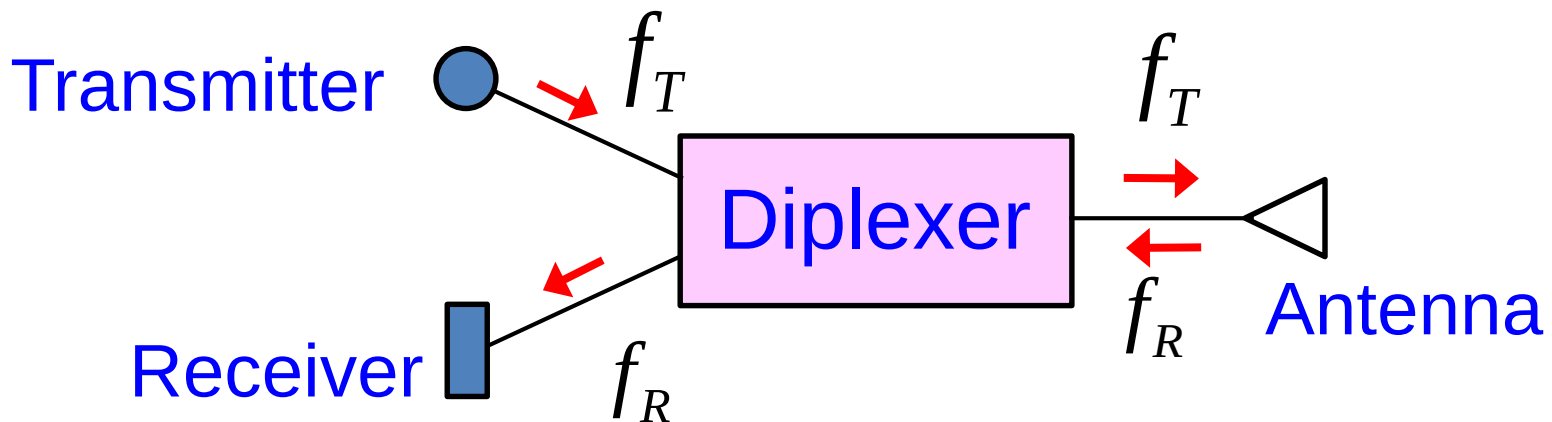Note: A diplexer can be used to transmit and receive two different channels with the same antenna (as with a duplexer), if the frequencies are separated enough.



Note:

This requires a high isolation between the transmit and receive ports, to avoid interference.

Isolator

An isolator is a two-port device that is nonreciprocal:

$$[S] = \begin{pmatrix} 0 & 0 \\ 1 & 0 \end{pmatrix}$$

- ❖ A wave coming in on port 1 goes through to port 2.
- ❖ A wave coming in on port 2 gets absorbed (does not go to port 1).



Frequency: 0.8 - 1 GHz

VSWR: 1.25

Isolation : 20 dB

Power: 2 W

Insertion loss: <0.4 dB

Length: 1.25 in

Width: 2 in


Height: 0.75 in

Temperature range: -20 – 60 deg C

Price: \$279.82

Circulator as Isolator

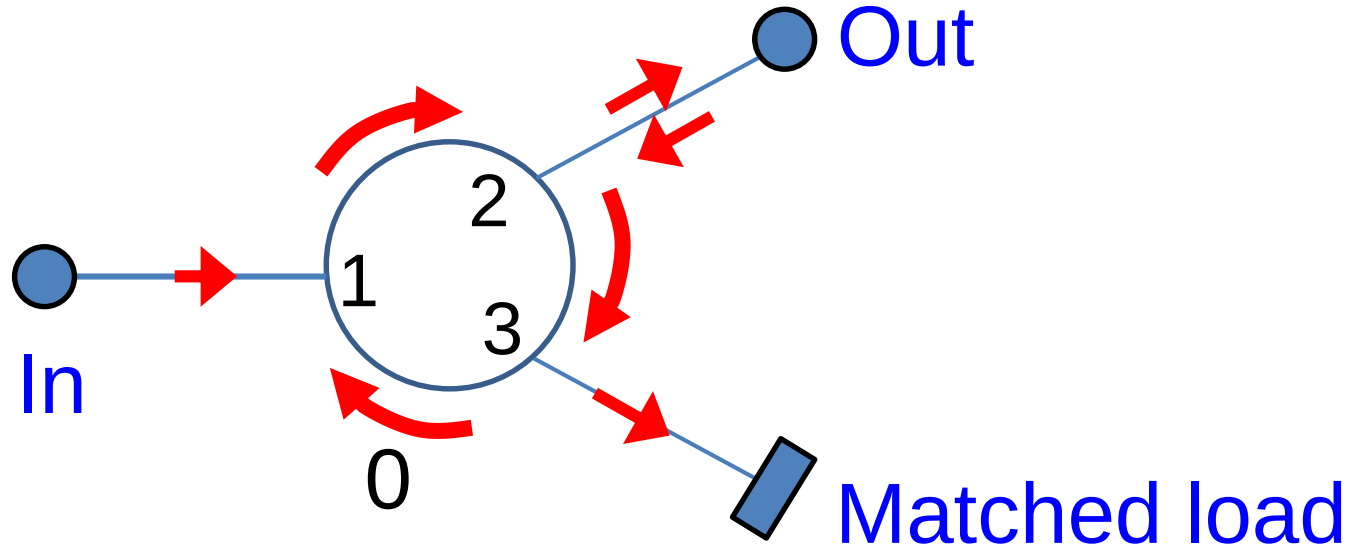A circulator can also be used to make an isolator:



- ❖ A signal from the input port goes to the output port.
- ❖ A signal from the output port does not get to the input port.

Circulator as Isolator (cont.)

A waveguide-based circulator with a matched load at port 3, acting as an isolator

